

HOW THE OUTPUT CAPACITOR CAN CAUSE INSTABILITY OF A POWER SUPPLY

Eleazar Falco
Application Engineer

WÜRTH ELEKTRONIK MORE THAN YOU EXPECT

AGENDA


- Review of feedback loop stability basics
- The output capacitor in a VM-CCM buck converter
 - The output capacitor in the power stage transfer function
 - Impact of output capacitor parameter variations
- Design cases with real measurements:
 - Adding/removing bulk capacitor
 - Same capacitance, different ESR
- A stable control-loop for any output capacitor?
- Q & A




REVIEW OF FEEDBACK LOOP STABILITY CONCEPTS

REVIEW OF BASICS - FEEDBACK LOOP STABILITY OF DC-DC CONVERTERS

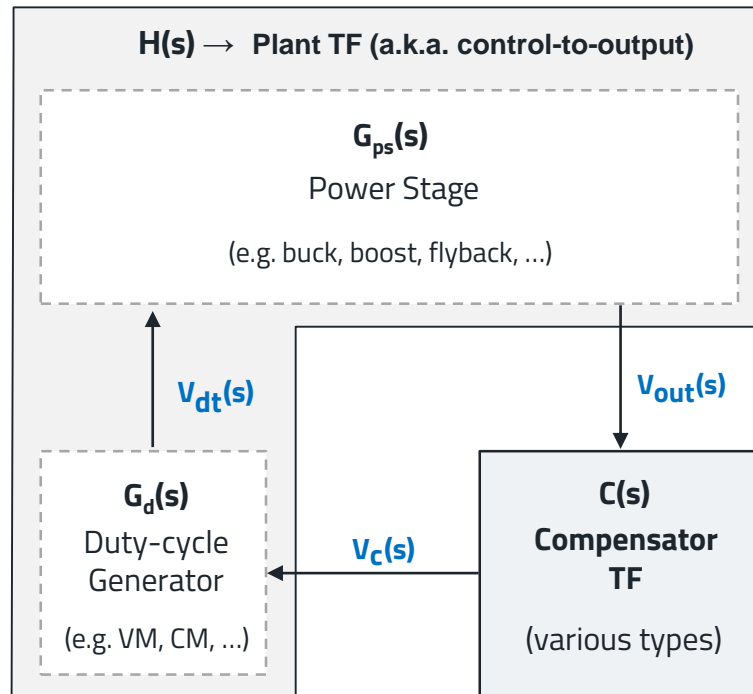The blocks in the control loop of a DC-DC converter



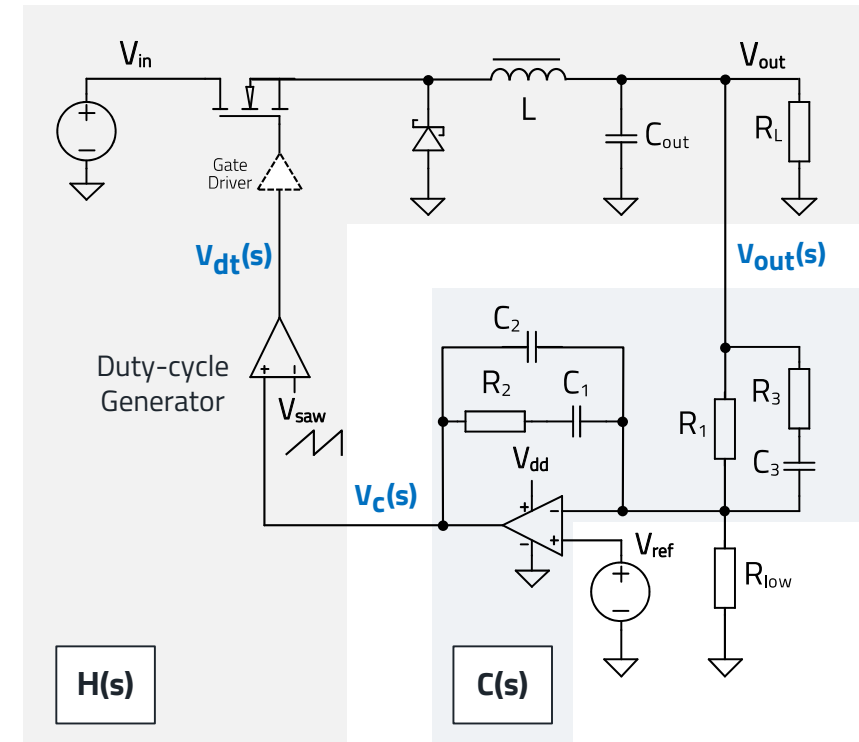
Voltage-mode buck converter with op-amp based type-3 compensator



REVIEW OF BASICS - FEEDBACK LOOP STABILITY OF DC-DC CONVERTERS

Open-loop transfer function and basic stability criteria

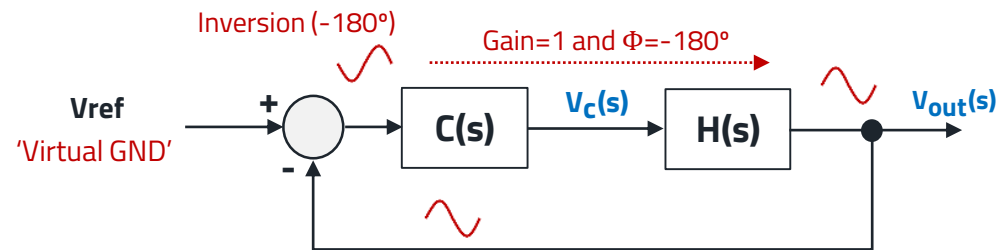Control-loop block diagram for AC (s-domain)




Open-loop TF $\rightarrow G_{OL}(s) = C(s) \cdot H(s)$

Stability criteria (only one crossover):

- For $|G_{OL}(f_c)| = 0$ dB (Gain=1) then:

$$\Phi(G_{OL}(f_c)) > -180^\circ$$

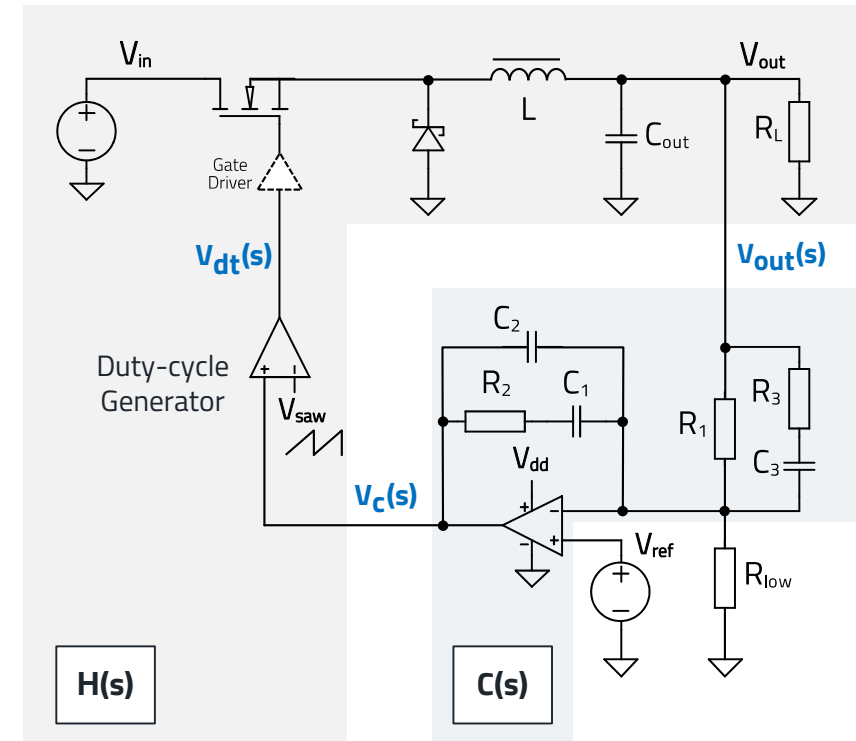Voltage-mode buck converter with op-amp based type-3 compensator




REVIEW OF BASICS - FEEDBACK LOOP STABILITY OF DC-DC CONVERTERS

Stability measurement: the voltage injection method

How we will be measuring it:

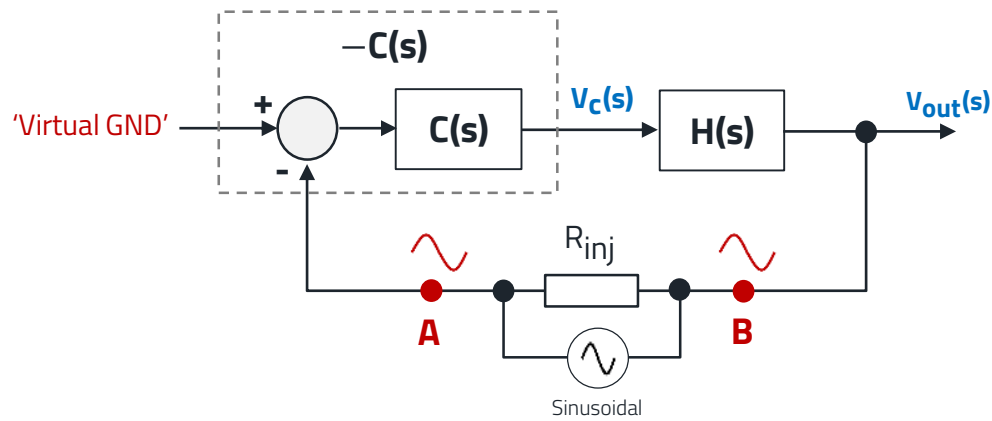
Inversion is included in the measured compensator frequency response (negative feedback). It cannot be separated.



$$\text{Open-loop TF} \rightarrow \mathbf{G_{OL}(s) = -C(s) \cdot H(s)}$$

$$\Phi(G_{OL}(f_c)) > -360^\circ \quad (\text{not } -180^\circ!)$$



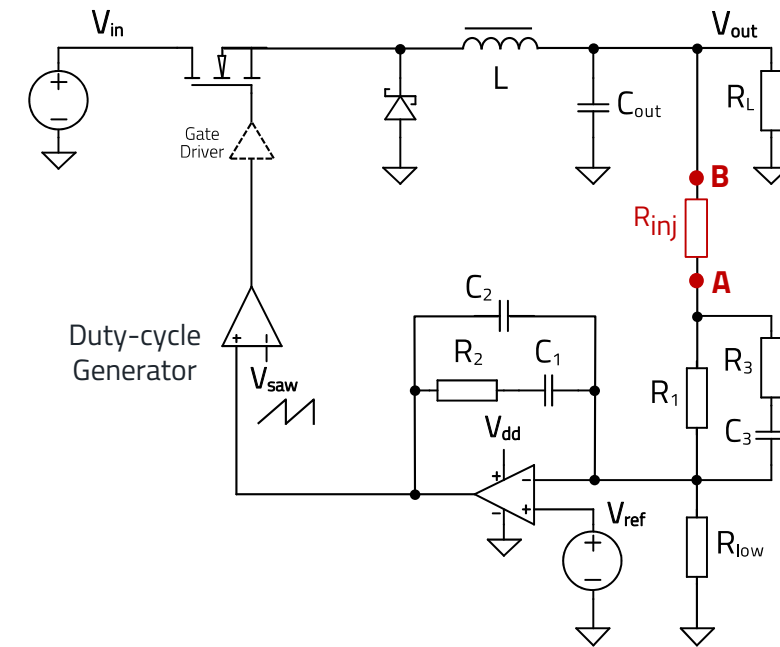
Voltage-mode buck converter with op-amp based type-3 compensator



(*) See for reference: *DC-DC Converter Stability Measurement, V3.3*, Application Note, Omicron Lab

REVIEW OF BASICS - FEEDBACK LOOP STABILITY OF DC-DC CONVERTERS

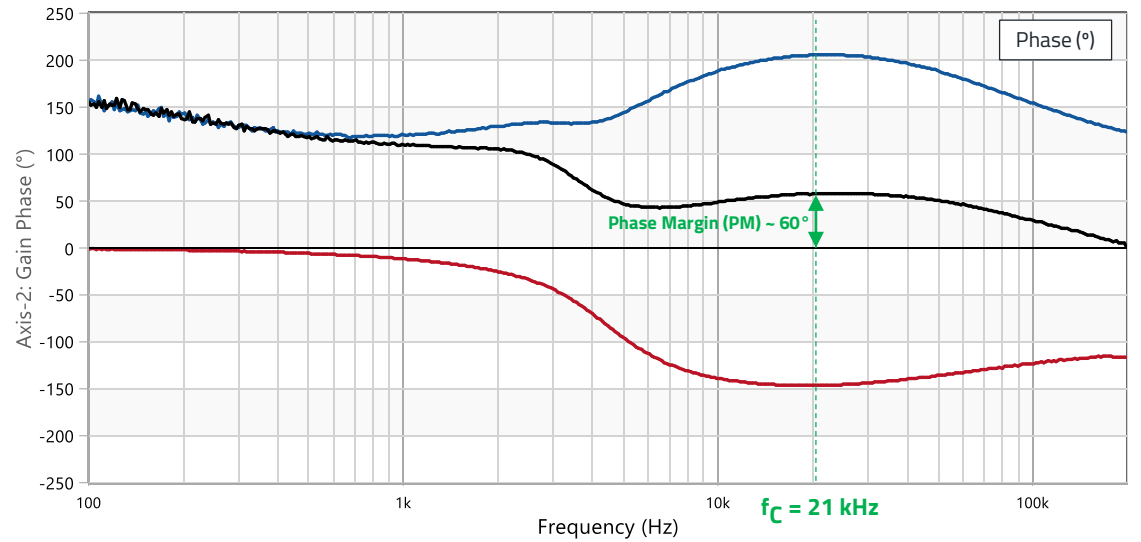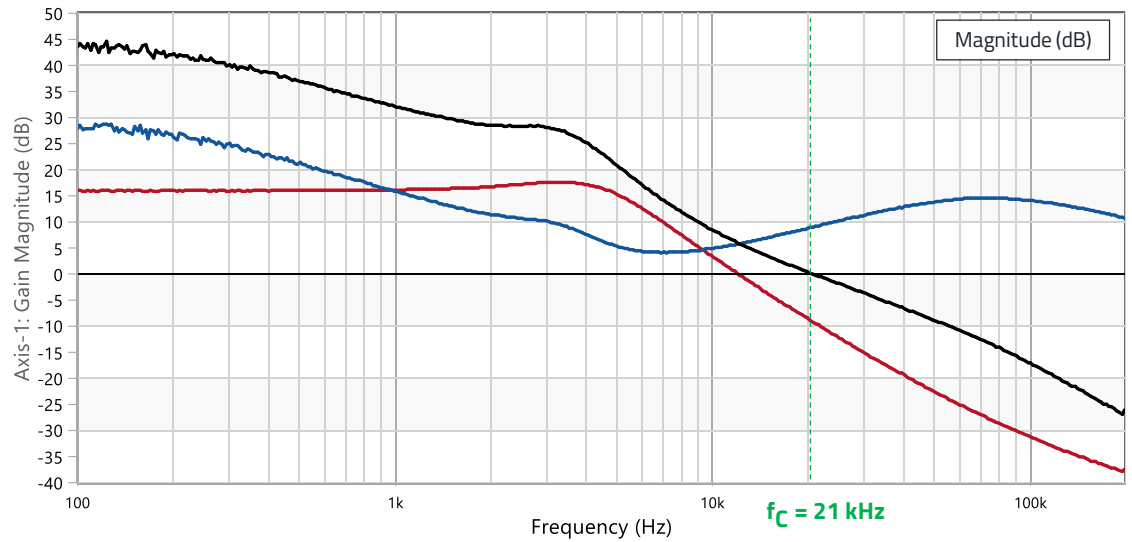
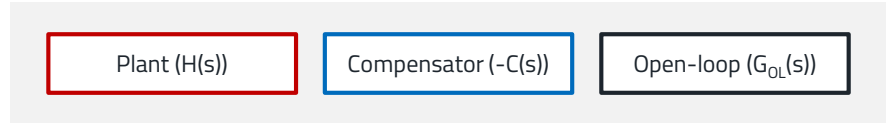
A measurement example: plant, compensator and open-loop response with stability margin



THE OUTPUT CAPACITOR IN A VM-CCM BUCK CONVERTER

THE OUTPUT CAPACITOR IN A VM-CCM BUCK CONVERTER

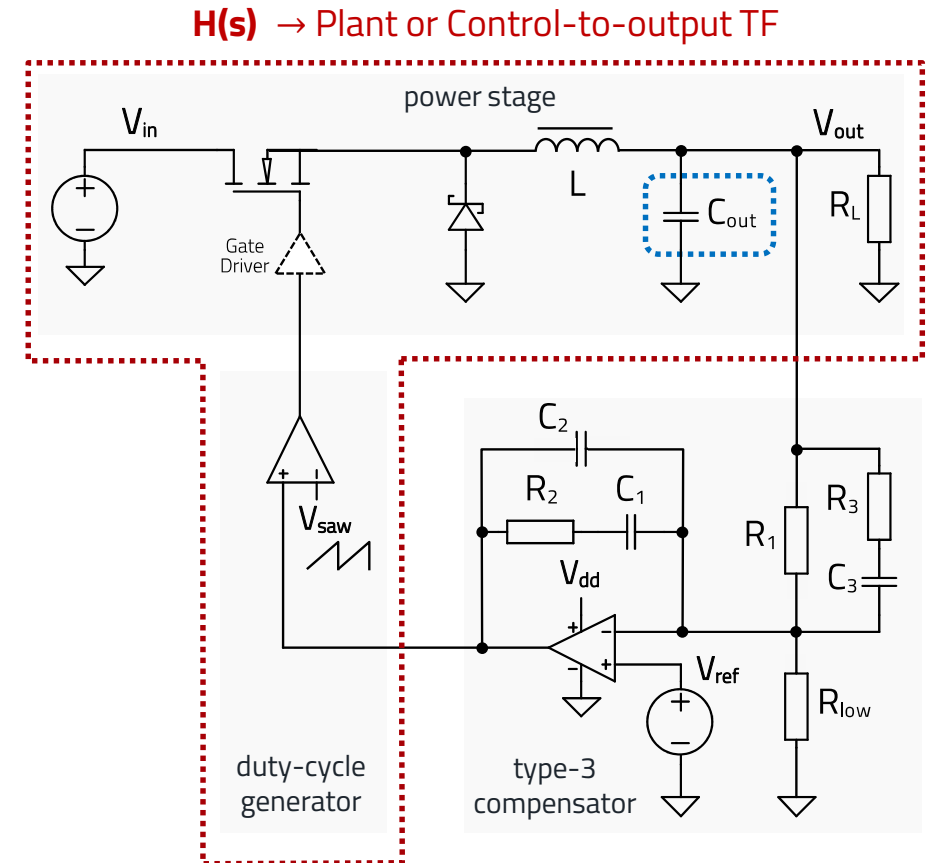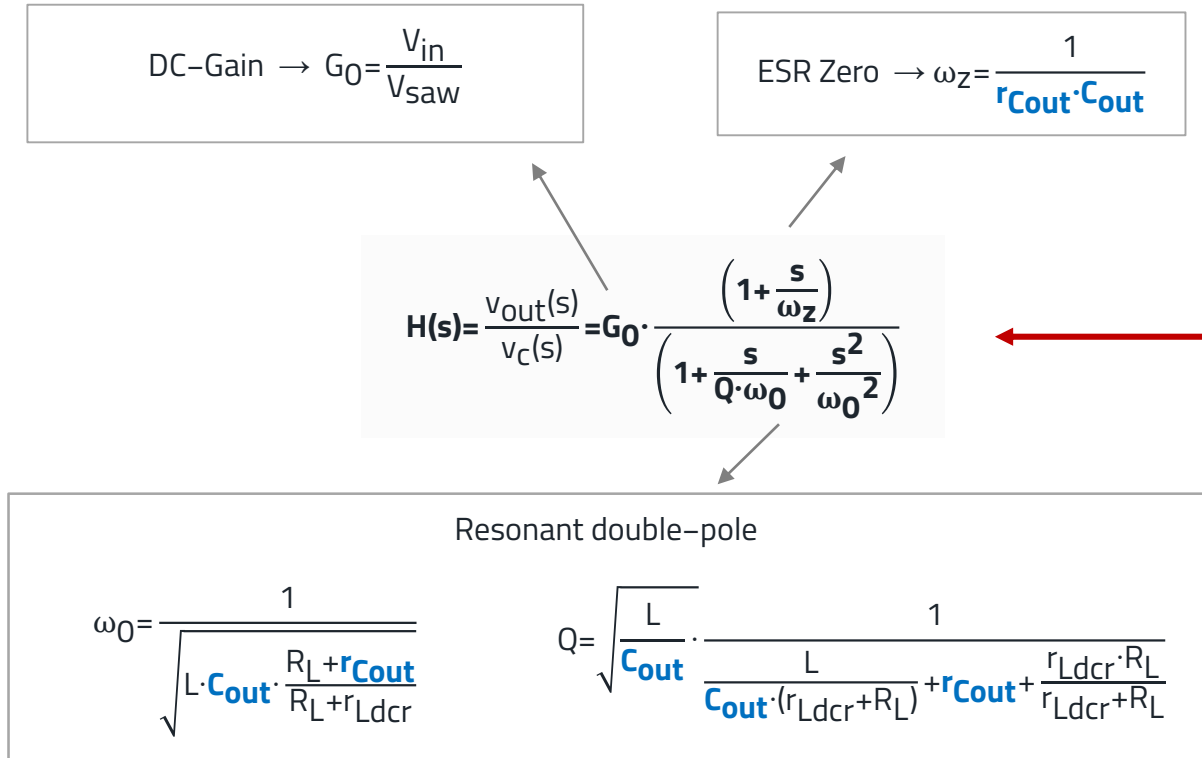
The plant or control-to-output transfer function of a VM-CCM Buck converter




(*) See for reference: *Switch-Mode Power Supplies: SPICE Simulations and Practical Designs*, Second Edition McGraw-Hill Professional, 2014, written by C. Basso

THE OUTPUT CAPACITOR IN A VM-CCM BUCK CONVERTER

The DC or low-frequency gain term

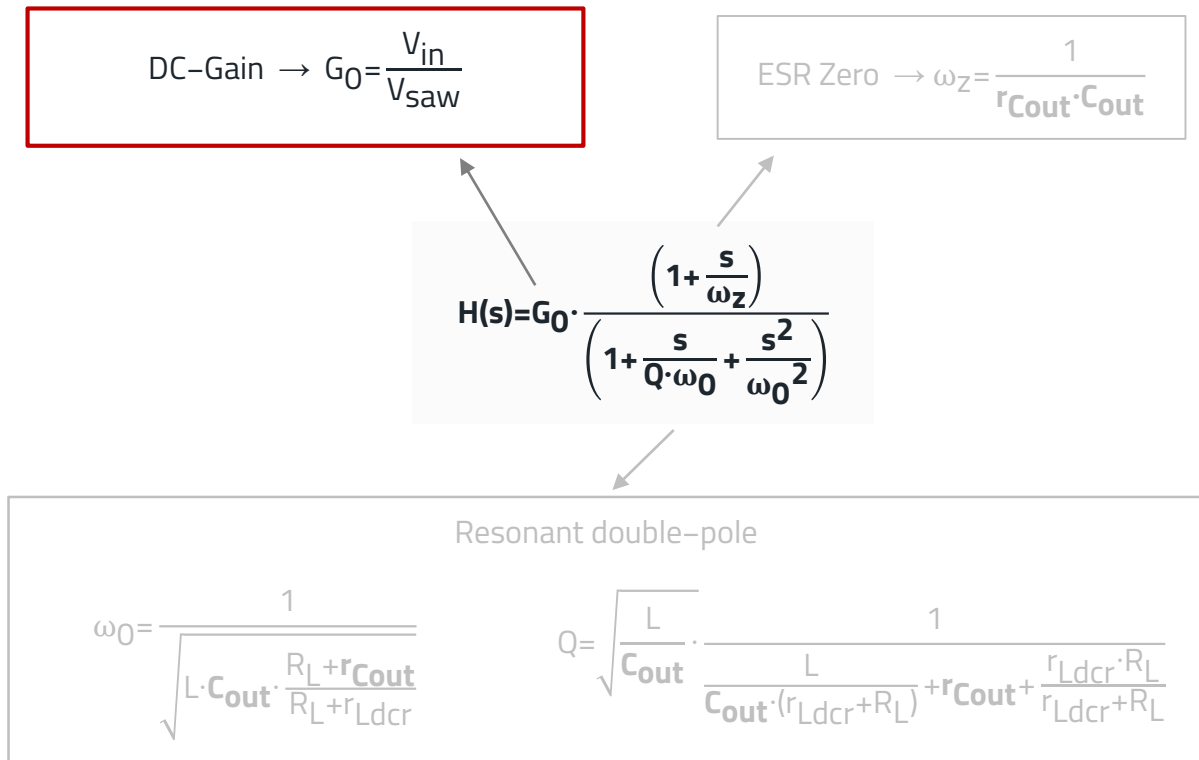


Example $G_0 = 21.2$ dB

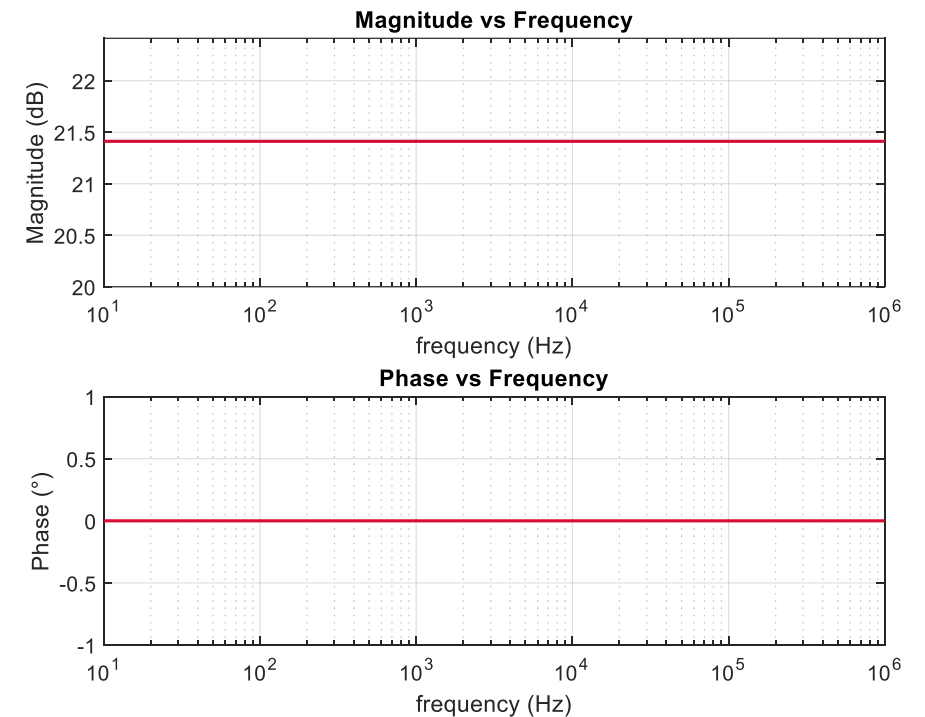


THE OUTPUT CAPACITOR IN A VM-CCM BUCK CONVERTER

The ESR zero


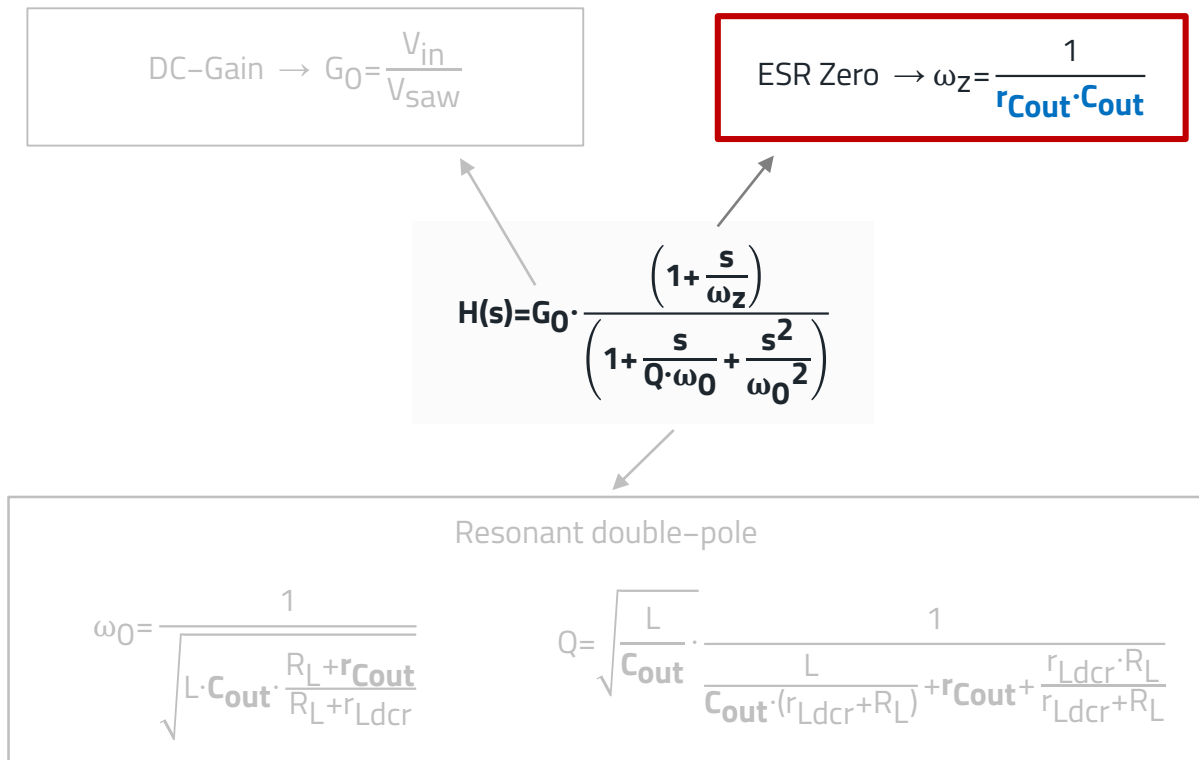


Example $f_z = 18 \text{ kHz}$

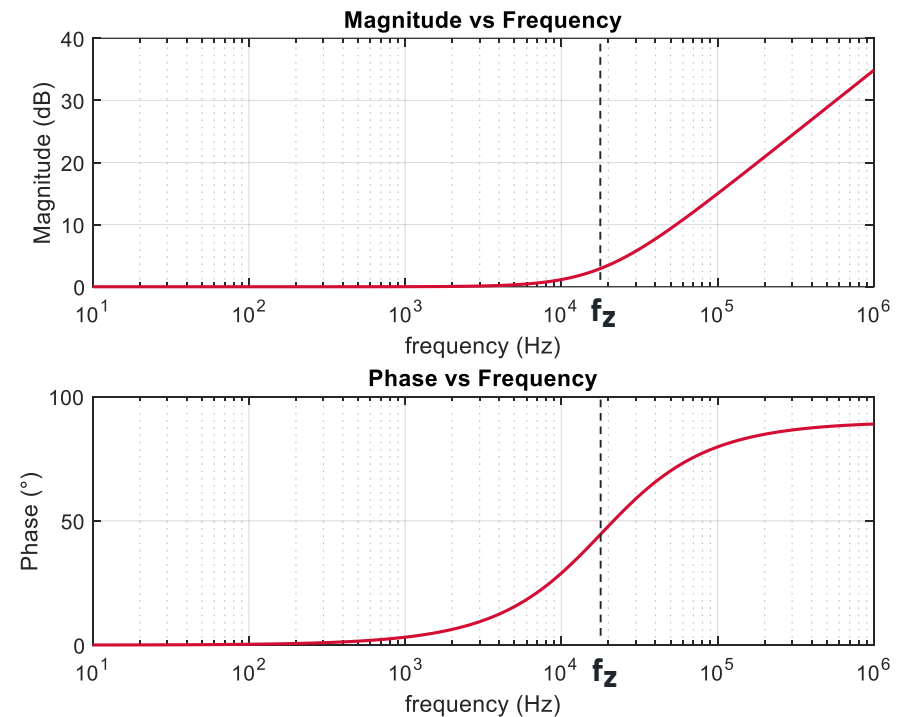


THE OUTPUT CAPACITOR IN A VM-CCM BUCK CONVERTER

The resonant double-pole

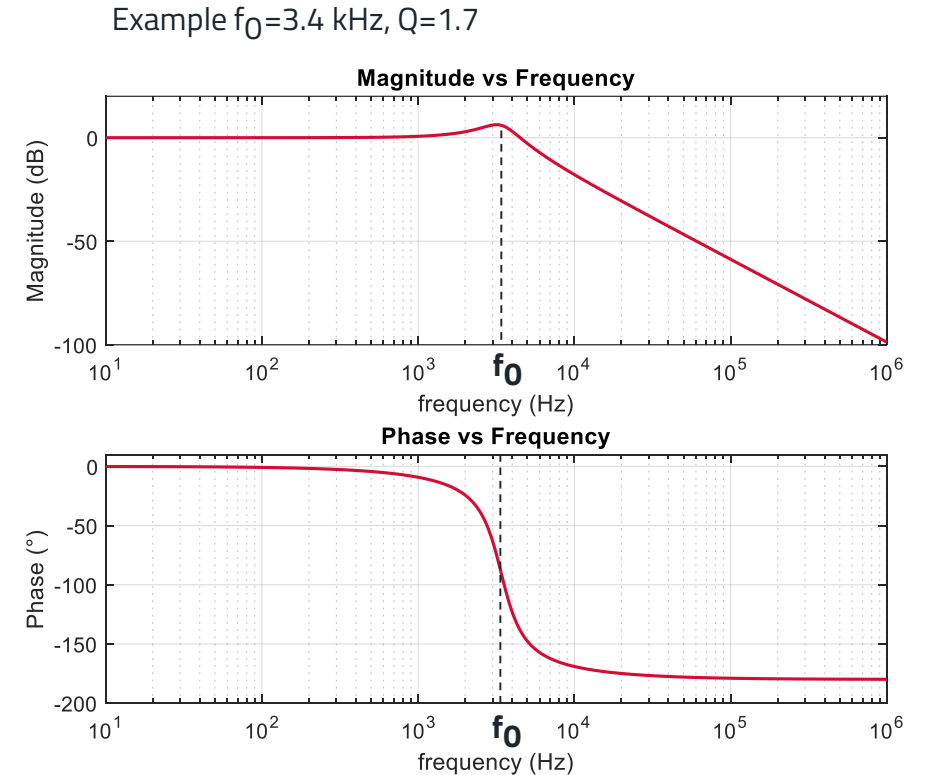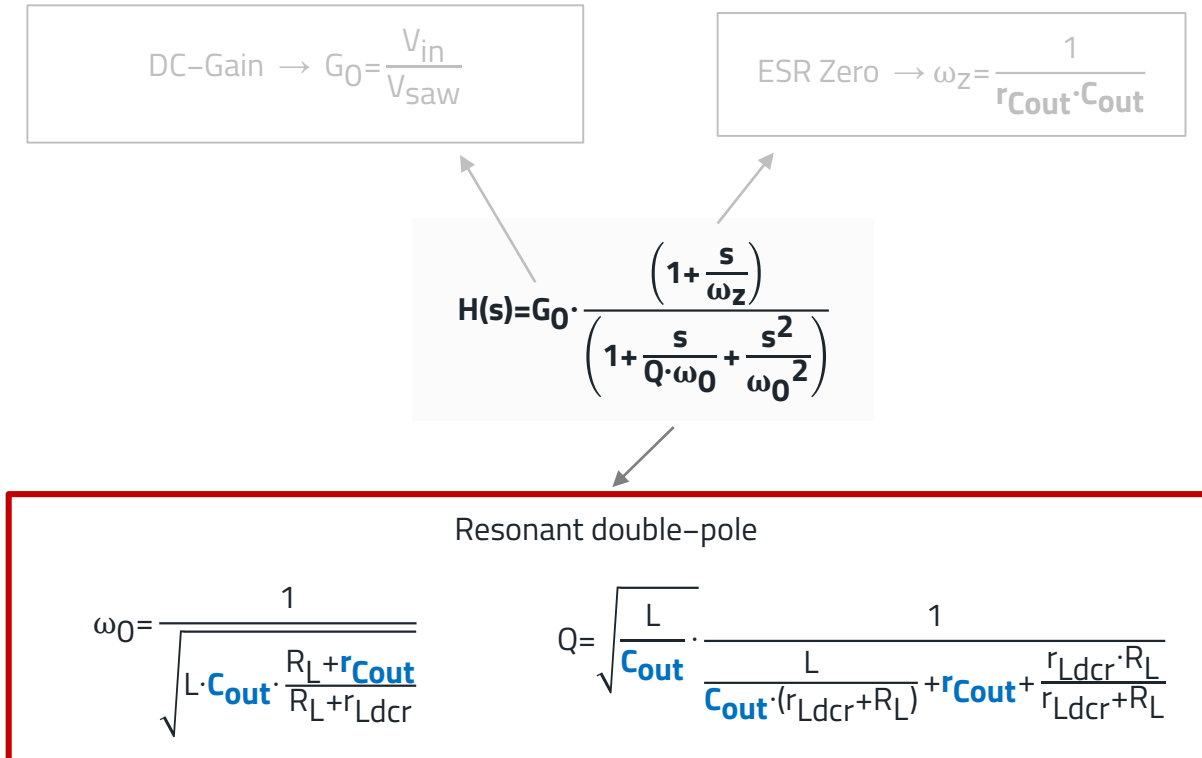

THE OUTPUT CAPACITOR IN A VM-CCM BUCK CONVERTER

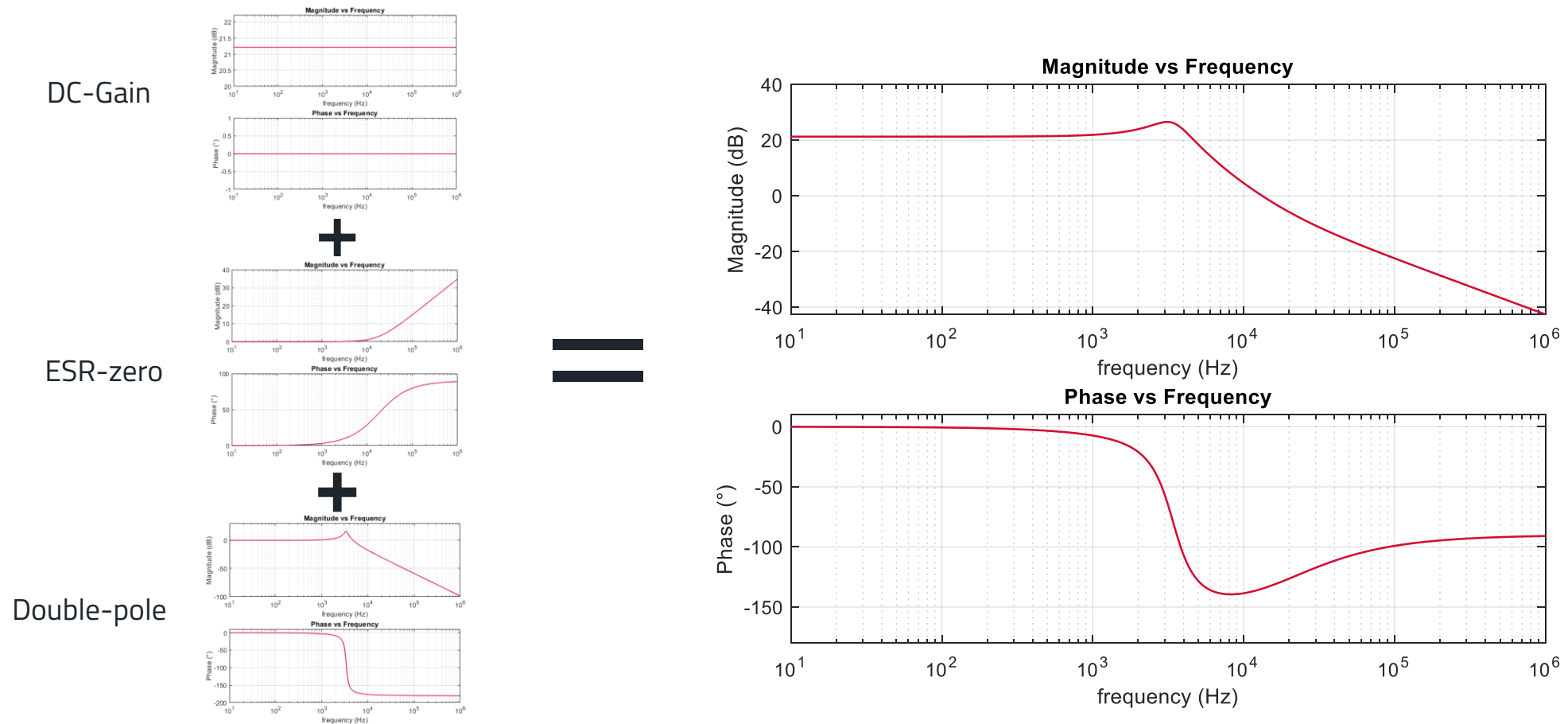Adding magnitude and phase curves of each term to obtain the plant frequency response




THE OUTPUT CAPACITOR IN A VM-CCM BUCK CONVERTER

VM-CCM buck specification used for the example

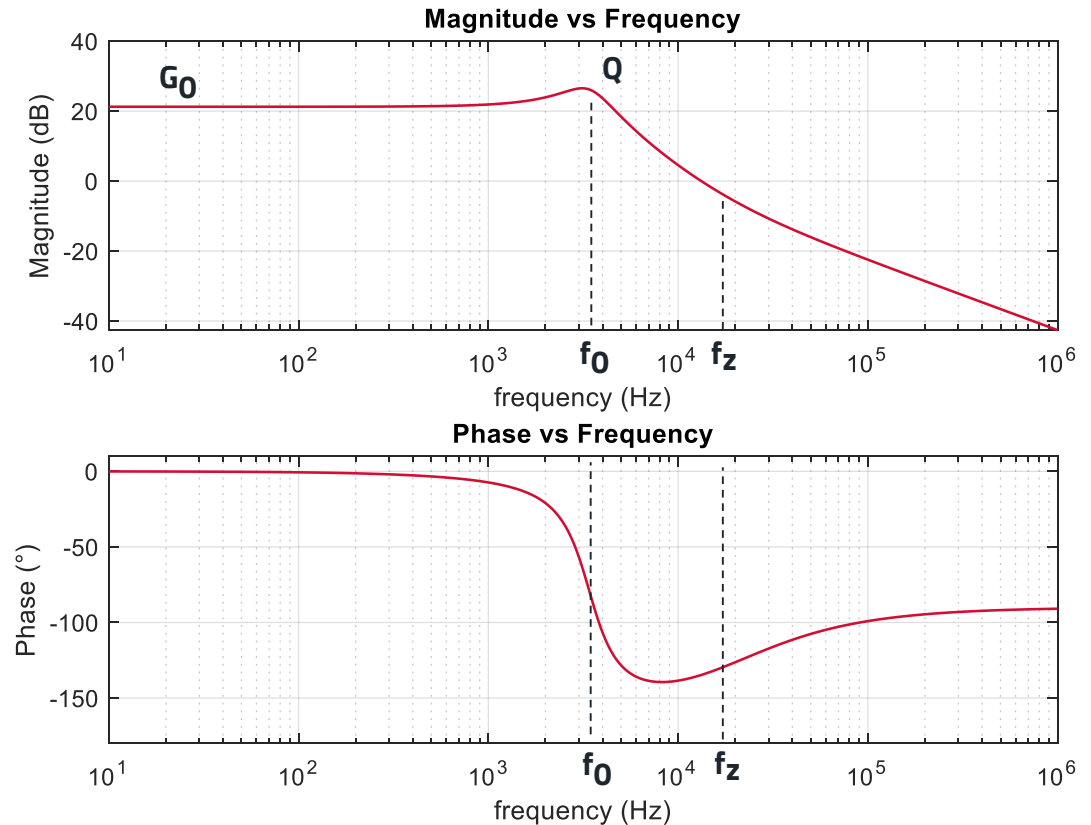Example Specification:

- $V_{in} = 24 \text{ V}$
- $V_{out} = 5 \text{ V}$
- $I_{out} = 2 \text{ A}$
- $F_{sw} = 500 \text{ kHz}$
- $L = 10 \text{ } \mu\text{H}$
- $\text{DCR} = 50 \text{ m}\Omega$
- $C_{out} = 220 \text{ } \mu\text{F}$
- $\text{ESR} = 40 \text{ m}\Omega$
- $V_{saw} = 2 \text{ V}$

$G_0 = 21.24 \text{ dB}$
 $f_z = 18 \text{ kHz}$
 $Q = 1.73$
 $f_0 = 3.4 \text{ kHz}$



THE OUTPUT CAPACITOR IN A VM-CCM BUCK CONVERTER

Selecting target crossover frequency range of the open-loop transfer function based on plant characteristic


- Target crossover frequency range

$$f_0/3 < f_c < f_{sw}/5$$

- In this example:

$$f_0 = 3.4 \text{ kHz and } f_{sw} = 500 \text{ kHz}$$
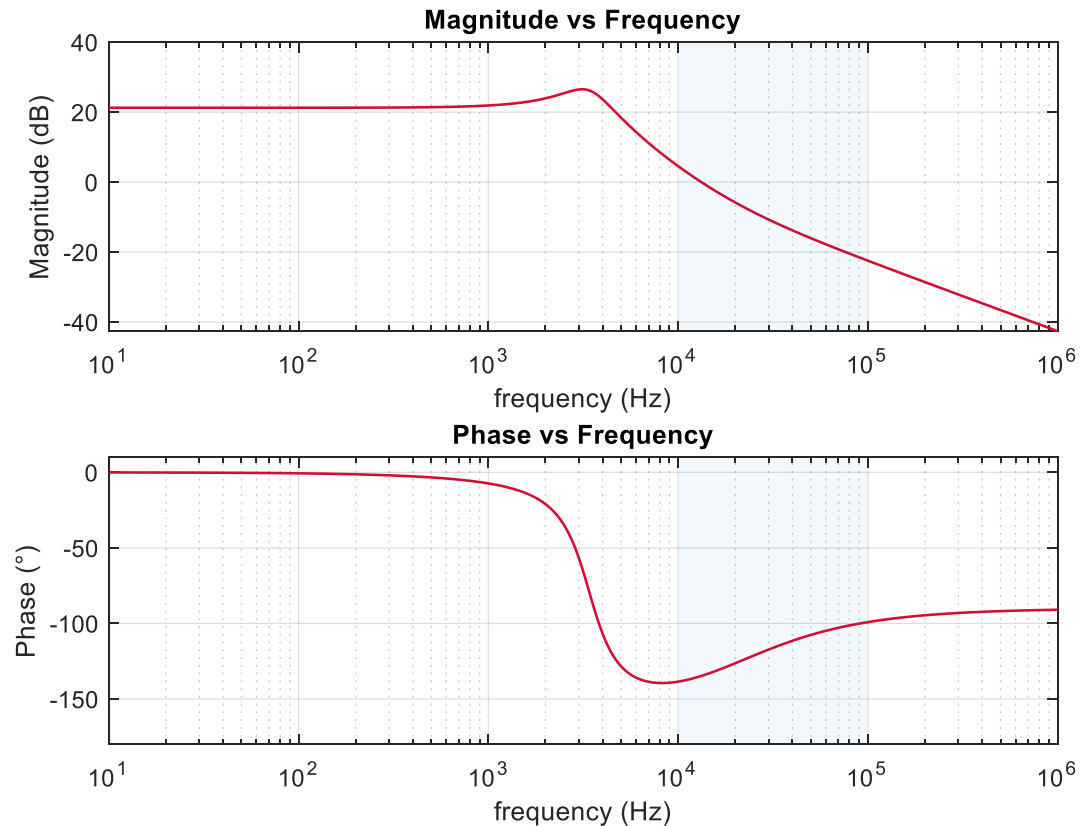
$$10 \text{ kHz} < f_c < 100 \text{ kHz}$$



HOW VARIATIONS IN OUTPUT CAPACITOR PARAMETERS IMPACT THE PLANT CHARACTERISTIC

HOW OUTPUT CAPACITOR VARIATIONS AFFECT THE PLANT RESPONSE

Example: Impact of capacitance variations with fixed ESR


Fixed ESR = 10 mΩ

$C_{out1} = 22 \mu\text{F}$ → $f_{z1}=723 \text{ kHz}$, $f_{o1}=11 \text{ kHz}$, $Q_1=1.65$

$C_{out2} = 100 \mu\text{F}$ → $f_{z2}=160 \text{ kHz}$, $f_{o2}=5.1 \text{ kHz}$, $Q_2=2.3$

$C_{out3} = 330 \mu\text{F}$ → $f_{z3}=48 \text{ kHz}$, $f_{o3}=2.8 \text{ kHz}$, $Q_3=2.1$

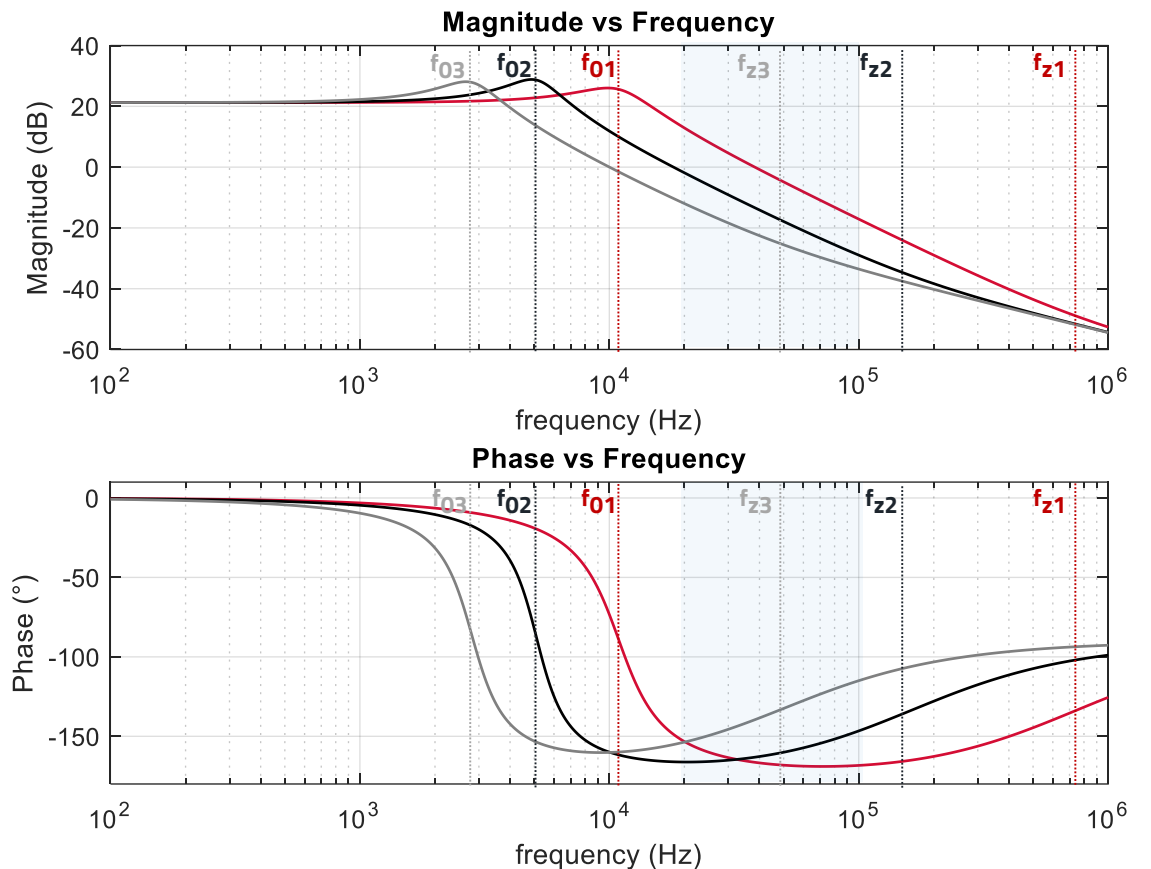Large change of f_z and f_o - Small change of Q
Gain difference up to ~ 25 dB (@20 kHz)
Phase difference up to ~ 65° (@100 kHz)



HOW OUTPUT CAPACITOR VARIATIONS AFFECT THE PLANT RESPONSE

Example: Impact of ESR variations with fixed capacitance

Fixed $C_{out} = 47 \mu\text{F}$

$\text{ESR}_1 = 10 \text{ m}\Omega \rightarrow f_{z1}=340 \text{ kHz}, f_{o1}=7.5 \text{ kHz}, Q_1=2.1$


$\text{ESR}_2 = 100 \text{ m}\Omega \rightarrow f_{z2}=34 \text{ kHz}, f_{o2}=7.2 \text{ kHz}, Q_2=1.5$

$\text{ESR}_3 = 300 \text{ m}\Omega \rightarrow f_{z3}=11.3 \text{ kHz}, f_{o3}=6.7 \text{ kHz}, Q_3=0.9$

Large change of f_z - Small change of f_o and Q

Gain difference up to $\sim 18 \text{ dB}$ (@ 100 kHz)

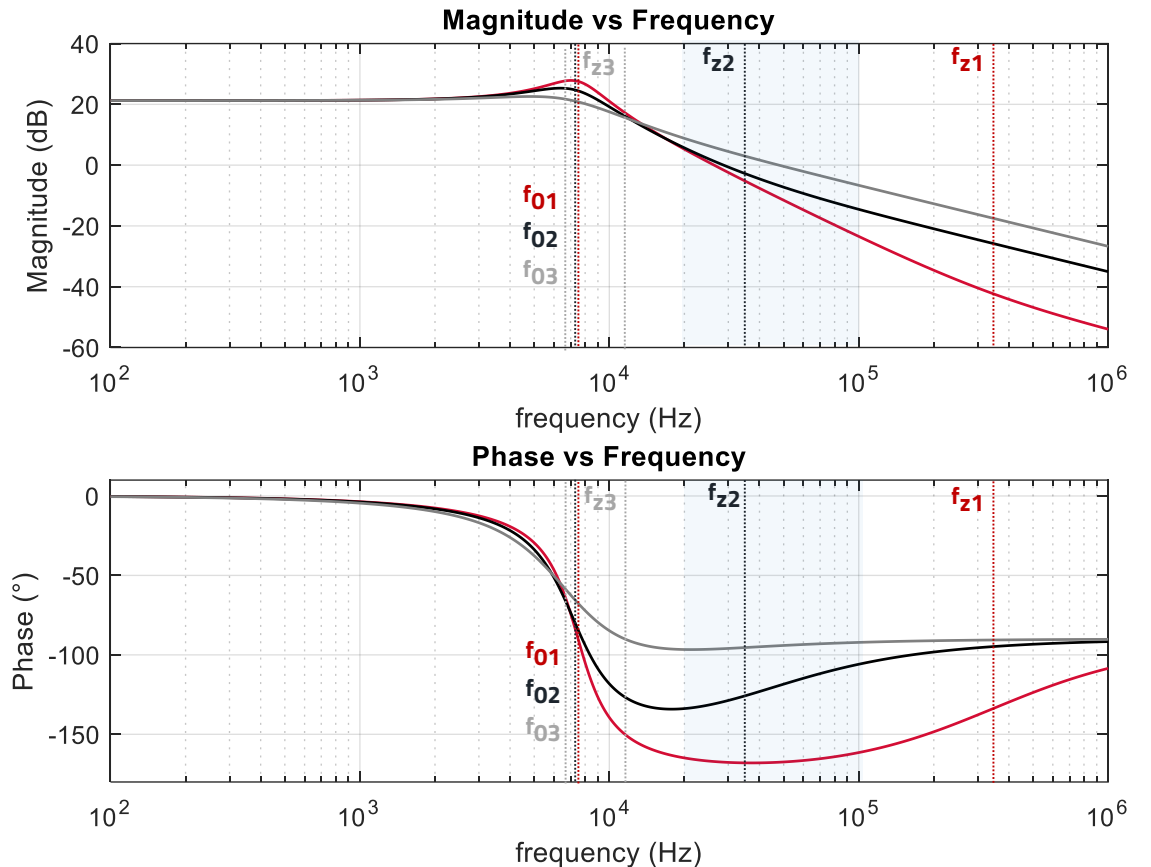Phase difference of $\sim 90^\circ$ (entire range)



DESIGN CASE EXAMPLE: IMPACT OF BULK CAPACITOR

DESIGN CASE EXAMPLE: IMPACT OF BULK CAPACITOR


Selecting output capacitor(s) for switching frequency ripple attenuation (Co1)

- $V_{in} = 12\text{ V}$
- $V_{out} = 5\text{ V}$
- $I_{out} = 4\text{ A}$
- $F_{sw} = 400\text{ kHz}$
- $L = 4.7\text{ }\mu\text{H}$ (MAPI 74438367047)
- $\Delta V_{out} < 0.5\%$ of V_{out} (i.e. 25 mV)


$$C_{o1} > \frac{\Delta I_L}{8 \cdot f_{sw} \cdot \Delta V_{out}} = \frac{1.7}{8 \cdot 400\text{k} \cdot 0.025} \approx 22\text{ }\mu\text{F}$$

- Co1 = 3 x WCAP-CSGP 885012209028
- Equivalent: 28 μF , 0.7 m Ω

REDEXPERT DATA: WCAP-CSGP-885012209028

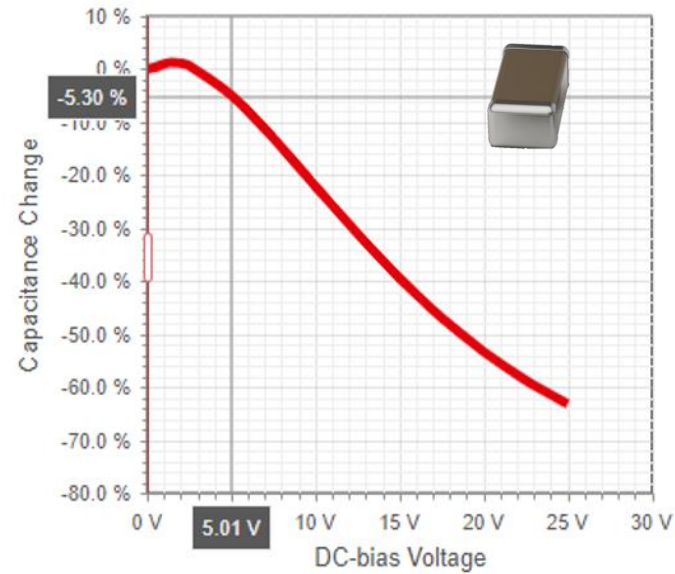
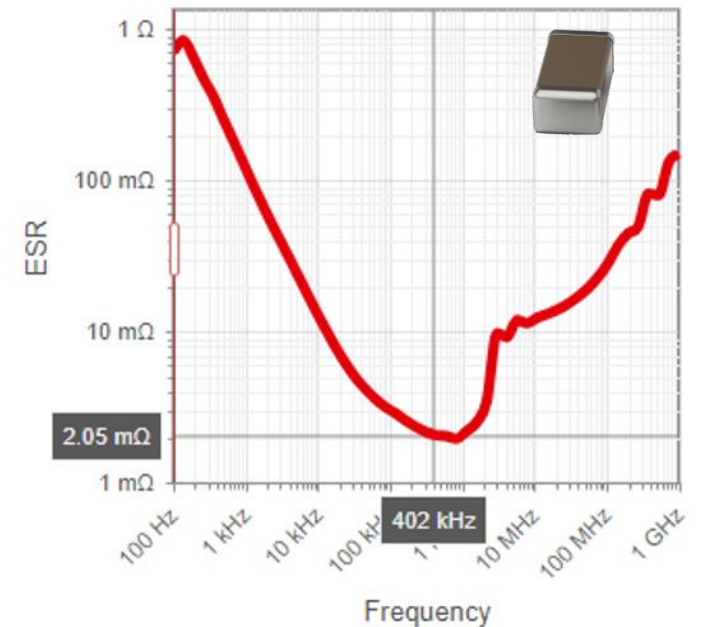
$$0.947 \cdot 10\mu\text{F} \approx 9.45\text{ }\mu\text{F}$$



DESIGN CASE EXAMPLE: IMPACT OF BULK CAPACITOR


Selecting output capacitor for transient response (a.k.a. bulk capacitor) (Co2)

- Transient Specification:
 - Load current step: 1.5 to 3.5 A (1 A/μs)
 - V_{out} undershoot < 100 mV
- Open-loop crossover frequency: 20 kHz


$$C_{o2_min} \approx \frac{\Delta I_{out}}{2 \cdot \pi \cdot f_c \cdot \Delta V_{out}} = \frac{2A}{2 \cdot \pi \cdot 20k \cdot 0.1V} \approx 160 \mu F$$

- Co2 = WCAP-HSAH 875585345004
- 220 μF, 16 V, 17 mΩ (@ 20 KHz)

REDEXPERT DATA: WCAP-HSAH-875585345004

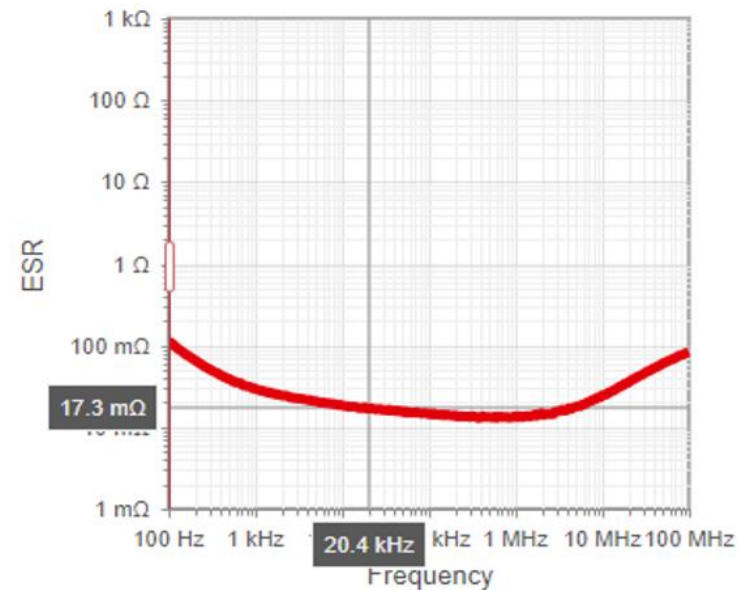

Hybrid-Polymer Capacitor

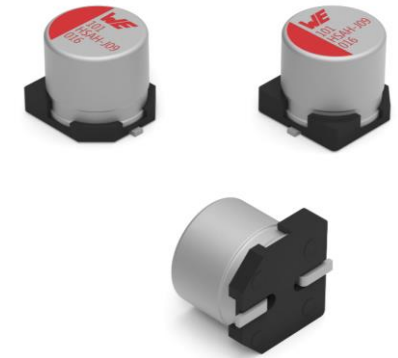


(*) See for reference: *Switch-Mode Power Supplies: SPICE Simulations and Practical Designs*, Second Edition McGraw-Hill Professional, 2014, written by C. Basso

DESIGN CASE EXAMPLE: IMPACT OF BULK CAPACITOR

The plant or control-to-output transfer function of VM-CCM Buck with Co1 and Co2 (bulk capacitor)

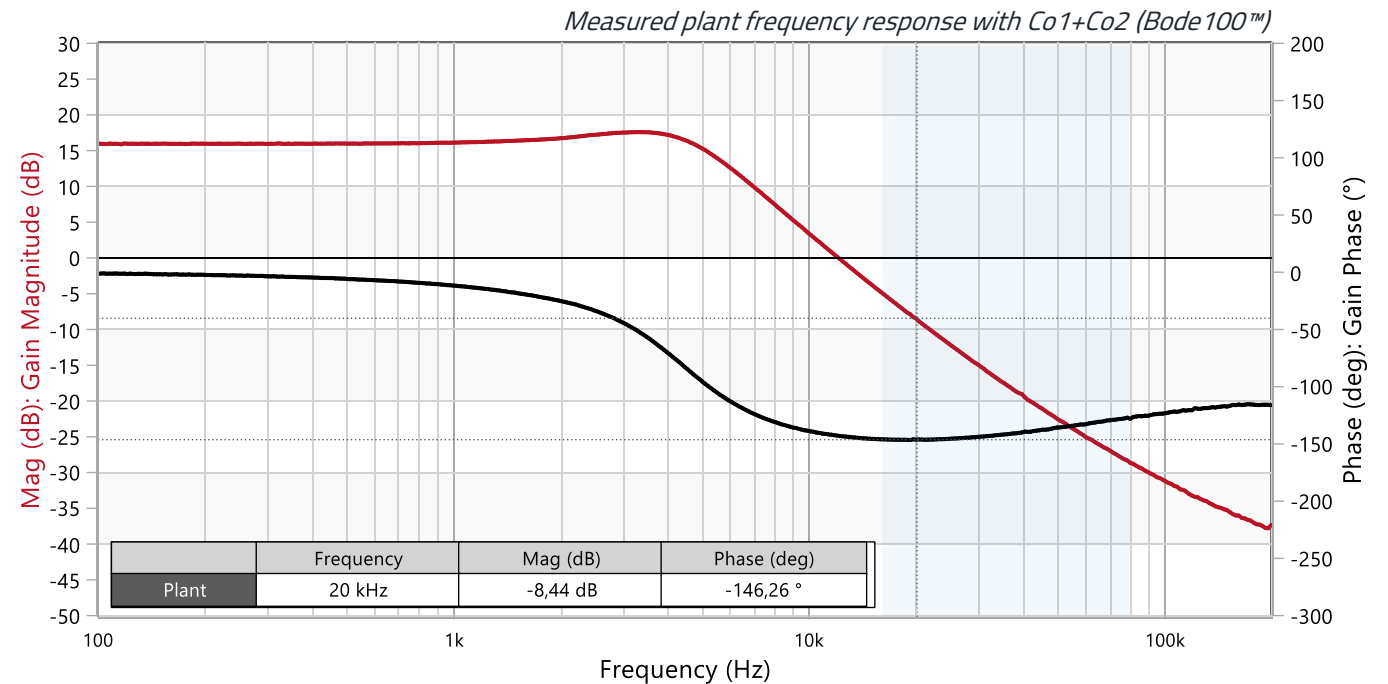- Bode plot of plant TF:
 - $f_z \approx 50$ kHz
 - $f_0 \approx 4$ kHz
 - $Q \approx 1.2$
- f_c selection range: 15 to 80 kHz
- Selected: 20 kHz
- Magnitude: -8.44 dB, Phase: -146°
- Target PM = 60°
- Required compensator phase lead: 116°
- Need of a type-3 compensator ...




DESIGN CASE EXAMPLE: IMPACT OF BULK CAPACITOR


Type-3 compensator design and frequency response

Compensator-1 circuit component values:

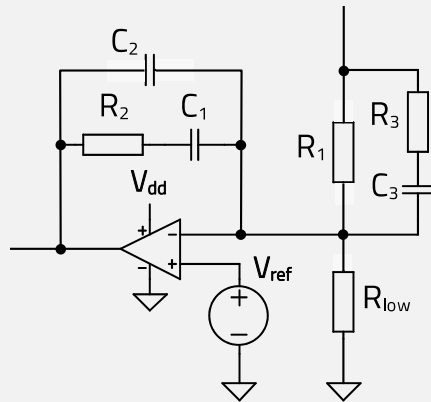- $R_1 = 73.2 \text{ k}\Omega$
- $R_{\text{low}} = 10 \text{ k}\Omega$
- $R_2 = 68 \text{ k}\Omega$
- $R_3 = 4.7 \text{ k}\Omega$
- $C_1 = 470 \text{ pF}$
- $C_2 = 33 \text{ pF}$
- $C_3 = 330 \text{ pF}$



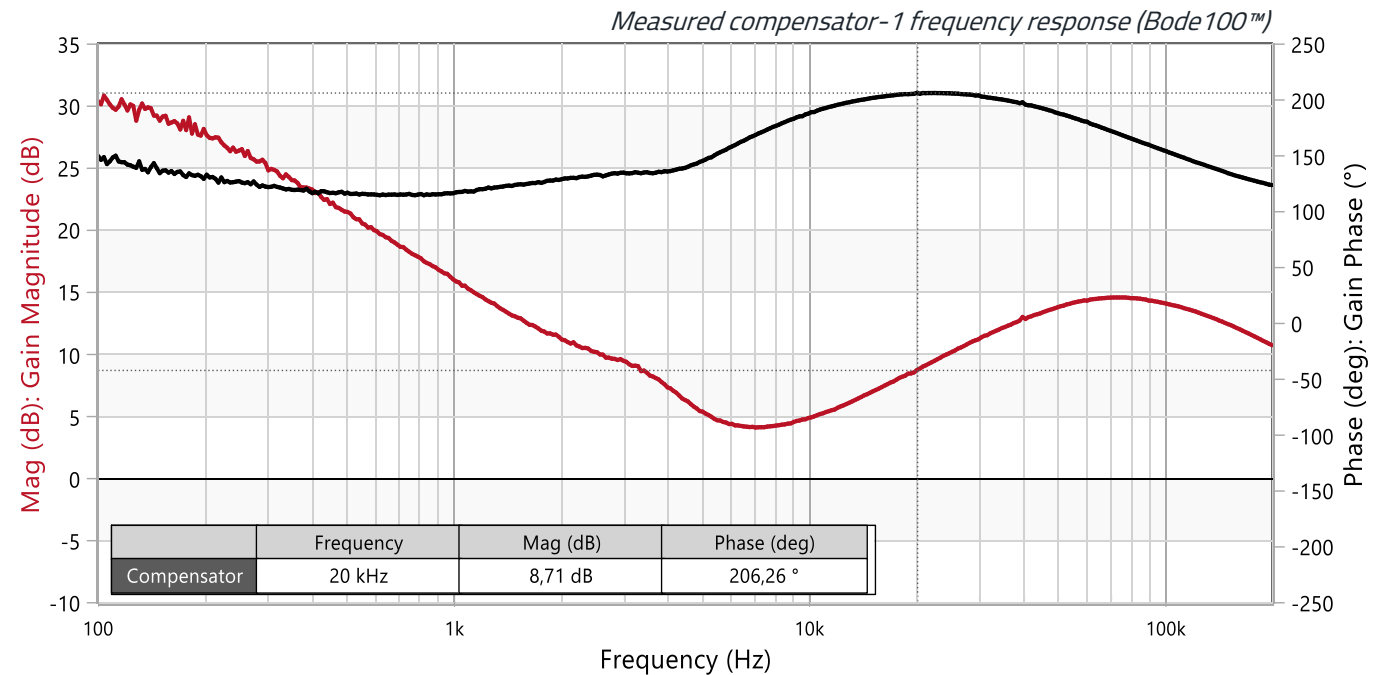Gain $\approx 8.7 \text{ dB}$, Phase $\approx 206^\circ$, Phase lead $\approx 116^\circ$




(*) See for reference: *Designing Control Loops for Linear and Switching Power Supplies: A Tutorial Guide*, Artech House, 2012, written by C. Basso

DESIGN CASE EXAMPLE: IMPACT OF BULK CAPACITOR


Open-loop response and stability margins: Co1+Co2 with compensator-1

Compensator-1 circuit component values:

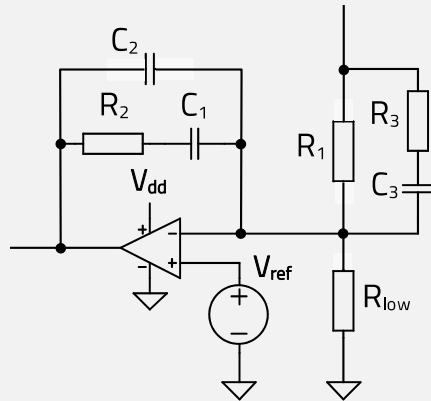- $R_1 = 73.2 \text{ k}\Omega$
- $R_{\text{low}} = 10 \text{ k}\Omega$
- $R_2 = 68 \text{ k}\Omega$
- $R_3 = 4.7 \text{ k}\Omega$
- $C_1 = 470 \text{ pF}$
- $C_2 = 33 \text{ pF}$
- $C_3 = 330 \text{ pF}$




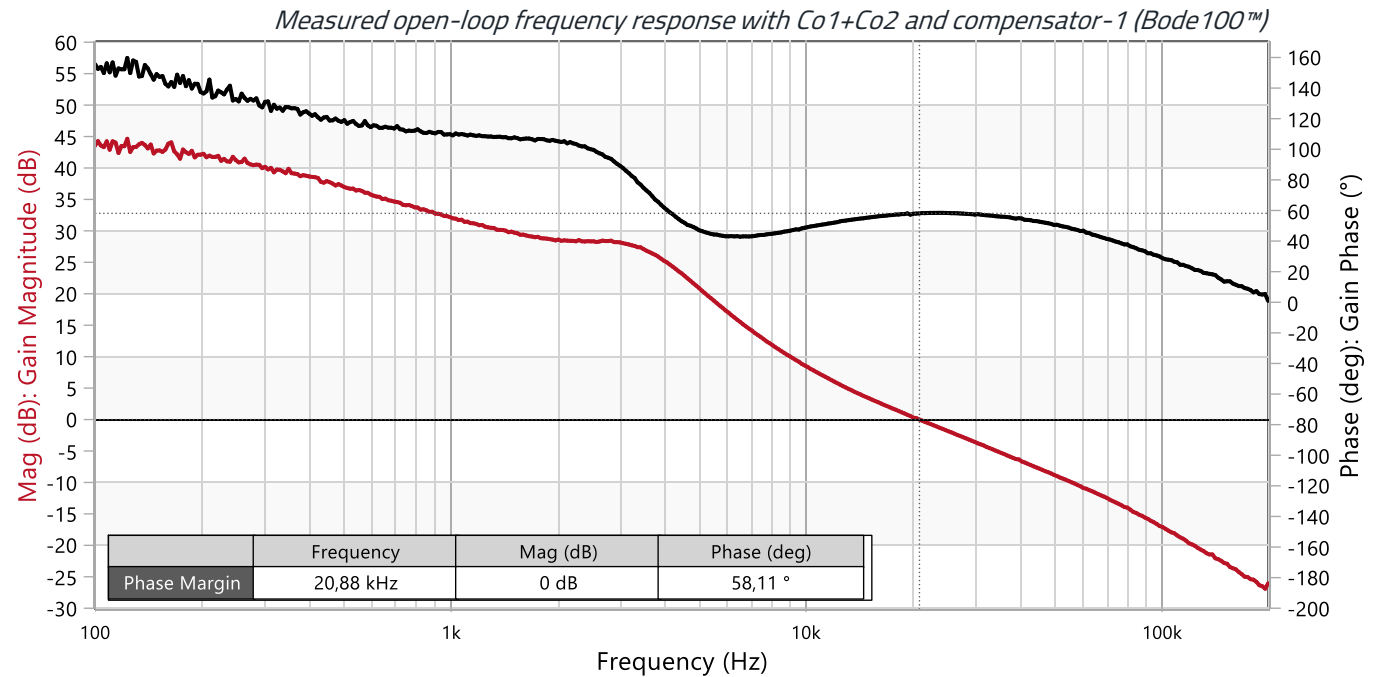$f_c \approx 21 \text{ kHz}$, $PM \approx 58^\circ$ and $GM \approx 25 \text{ dB}$




DESIGN CASE EXAMPLE: IMPACT OF BULK CAPACITOR

Buck converter board and load transient response: Co1+Co2 with compensator-1

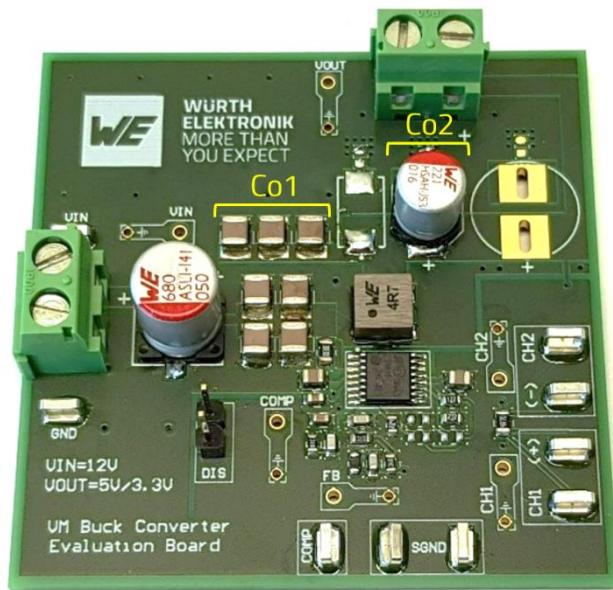

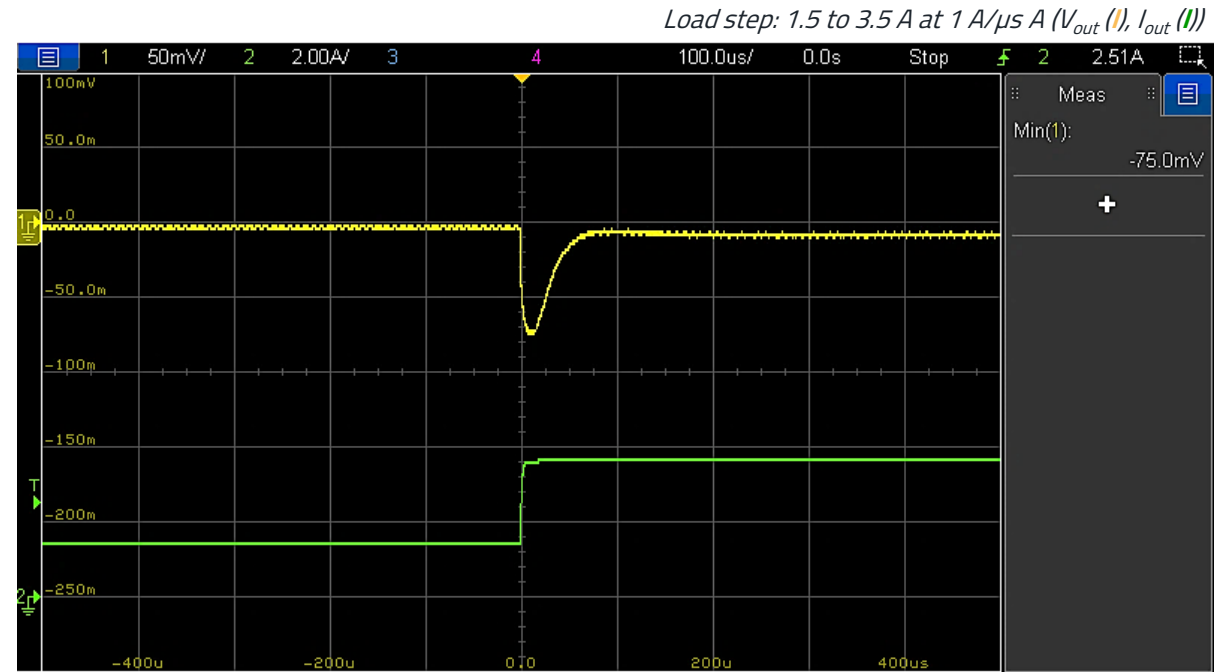Prototype VM-CCM buck board with Co1 and Co2




V_{out} undershoot of 75 mV (maximum was 100 mV)



DESIGN CASE EXAMPLE: IMPACT OF BULK CAPACITOR

Impedance curves: Co2 does not affect switching frequency ripple

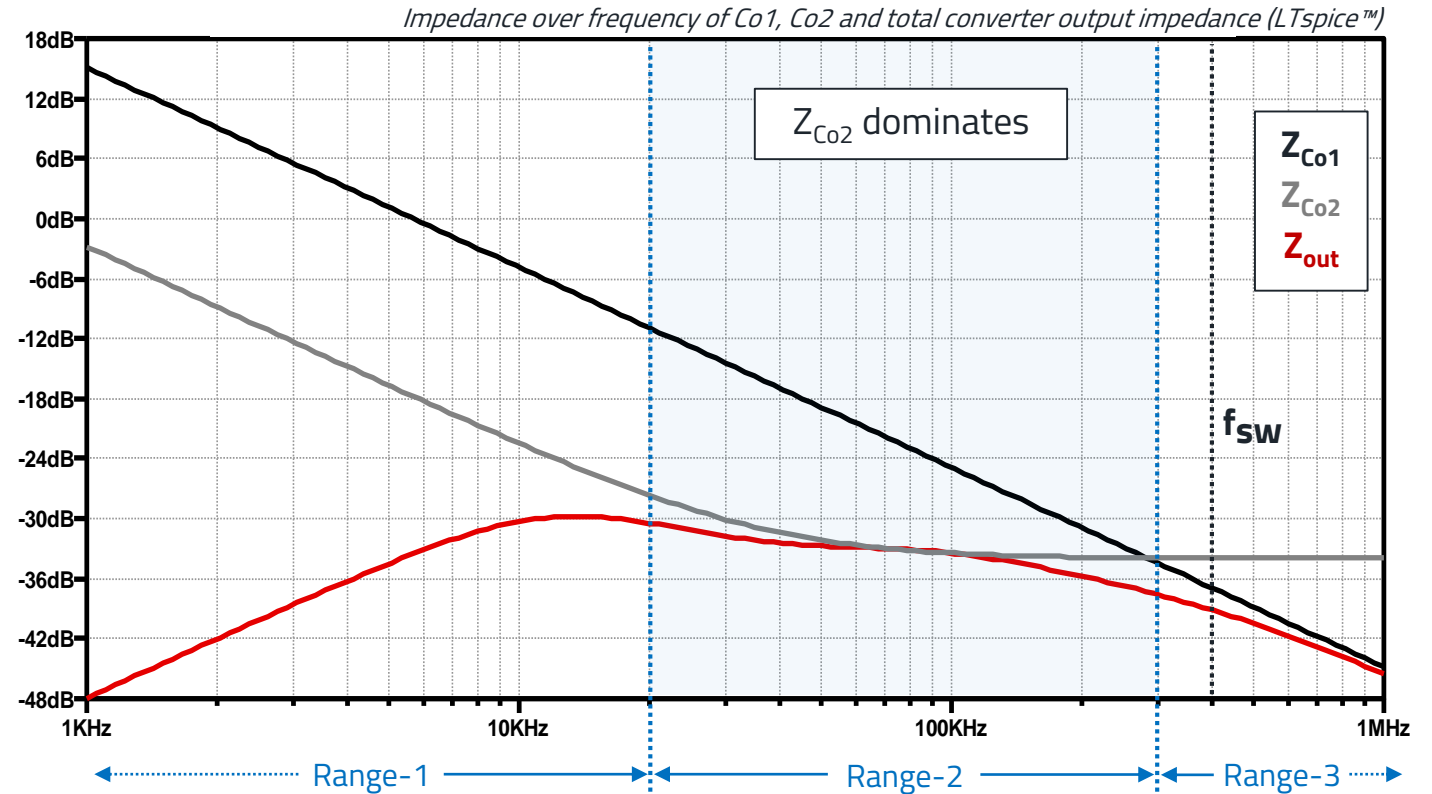- Range-1: $f < f_c$ (=20 kHz)
 - Z_{out} set by closed control loop
- Range-2: $20 \text{ kHz} < f < 300 \text{ kHz}$
 - Z_{out} set by Co2
- Range-3: $f > 300 \text{ kHz}$
 - Z_{out} set by Co1
- $f_{sw} = 400 \text{ kHz} \rightarrow Z_{Co1}$
- Co2 does not almost affect ΔV_{out}
- Relaxed transient requirement:
 - **Co2 can be removed**




DESIGN CASE EXAMPLE: IMPACT OF BULK CAPACITOR

Removing Co2 with compensator-1: unstable operation



Co2 removed ...

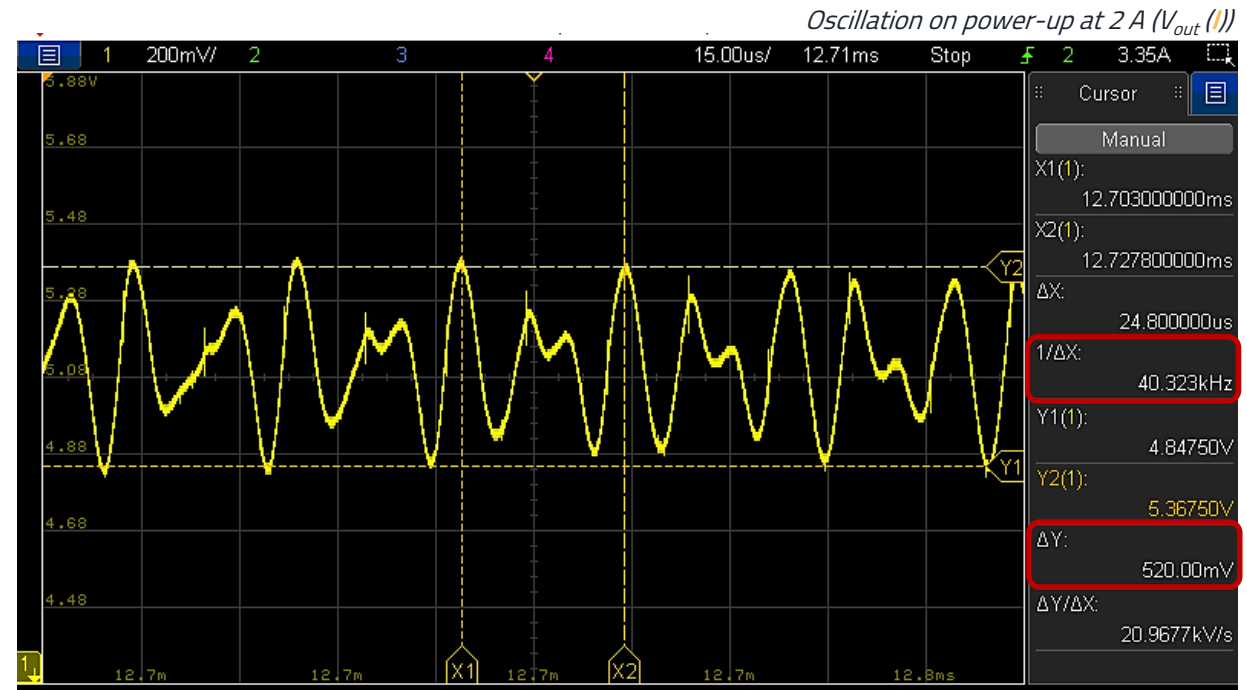- Oscillation at 80 kHz
- Around 520 mV amplitude
- Erratic behavior (turn switching on/off)



DESIGN CASE EXAMPLE: IMPACT OF BULK CAPACITOR

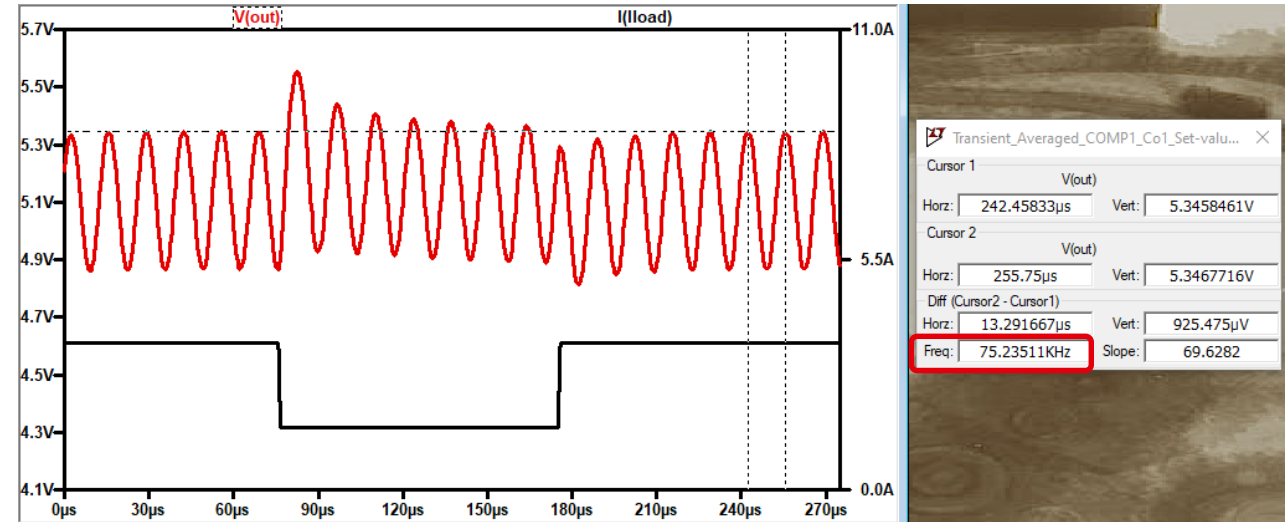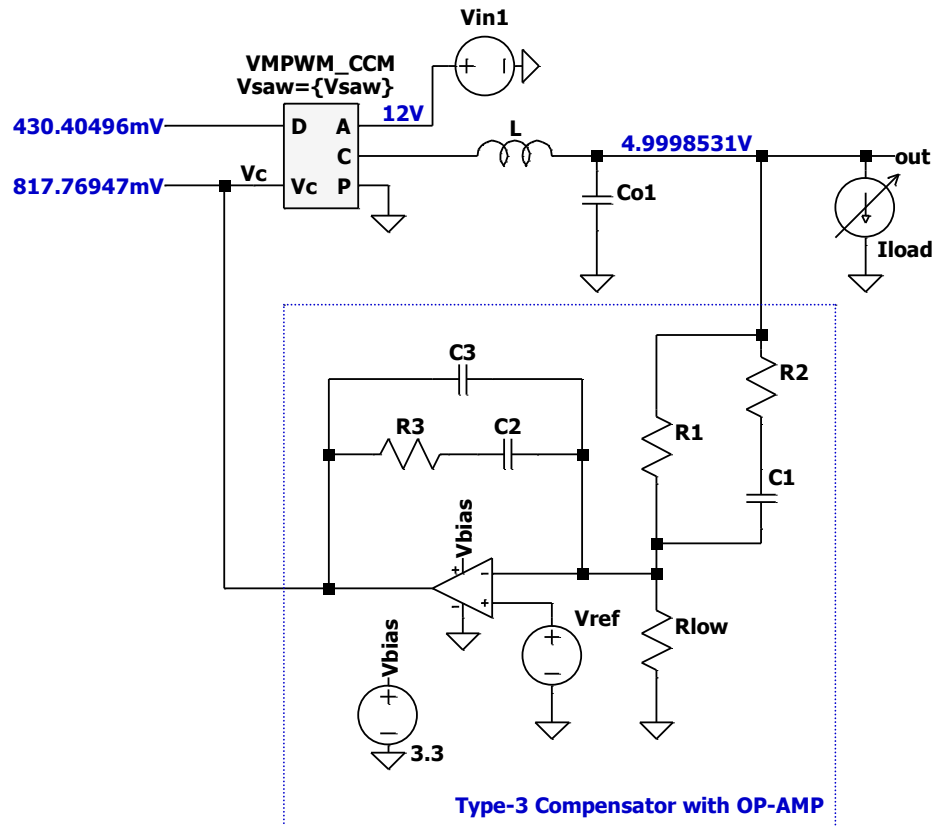LTspice™ transient simulation with averaged PWM switch model: unstable operation





- Oscillation at ~ 75 kHz
- Amplitude ~ 550 mV

In line with measurement ...

(*) See for reference: *Switch-Mode Power Supplies: SPICE Simulations and Practical Designs*, Second Edition McGraw-Hill Professional, 2014, written by C. Basso

DESIGN CASE EXAMPLE: IMPACT OF BULK CAPACITOR

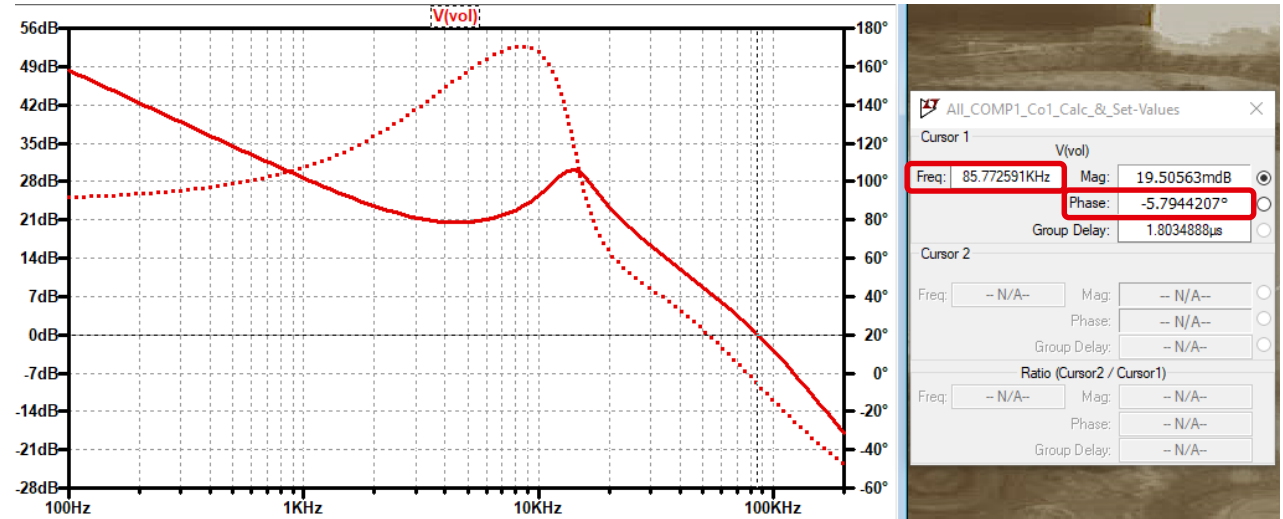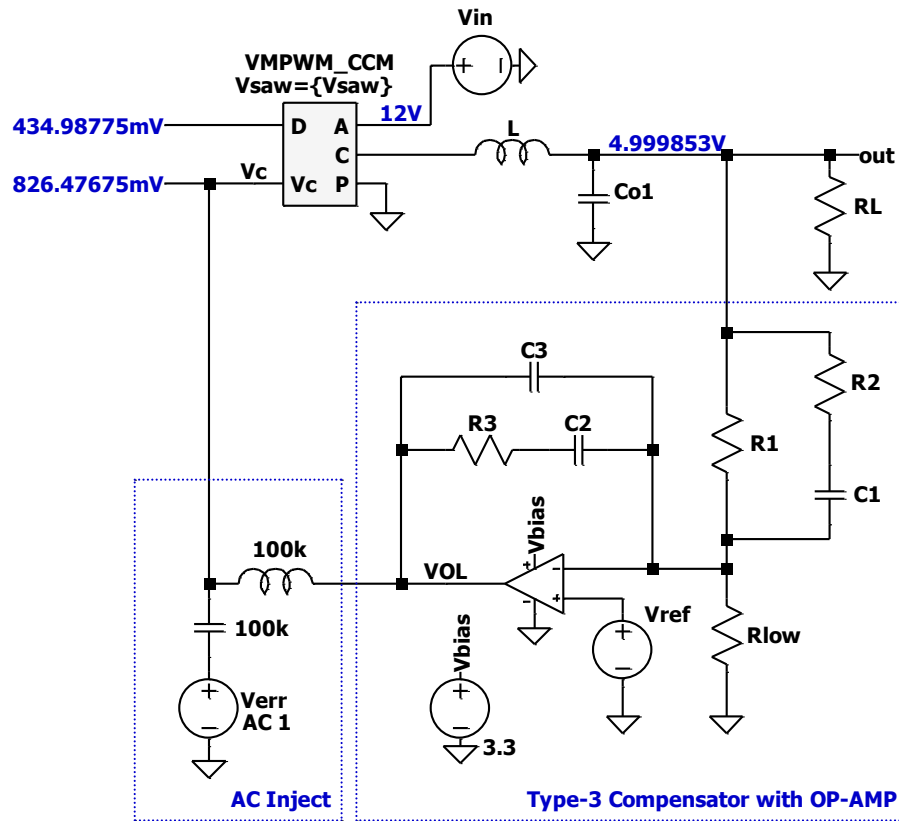LTspice™ .AC simulation with averaged PWM switch model: open-loop response confirms instability



- $f_c \sim 85$ kHz
- $PM \sim -6^\circ$

Unstable control loop confirmed ...

(*) See for reference: *Switch-Mode Power Supplies: SPICE Simulations and Practical Designs*, Second Edition McGraw-Hill Professional, 2014, written by C. Basso

DESIGN CASE EXAMPLE: IMPACT OF BULK CAPACITOR

How did the plant response change?

Plant TF with **Co1+Co2**

$$f_{z1} \approx 50 \text{ kHz}$$

$$f_{o1} \approx 4 \text{ kHz}$$


$$Q_1 \approx 1.2$$

Plant TF with **Co1**

$$f_{z2} \approx 8 \text{ MHz}$$

$$f_{o2} \approx 14 \text{ kHz}$$

$$Q_2 \approx 2.5$$

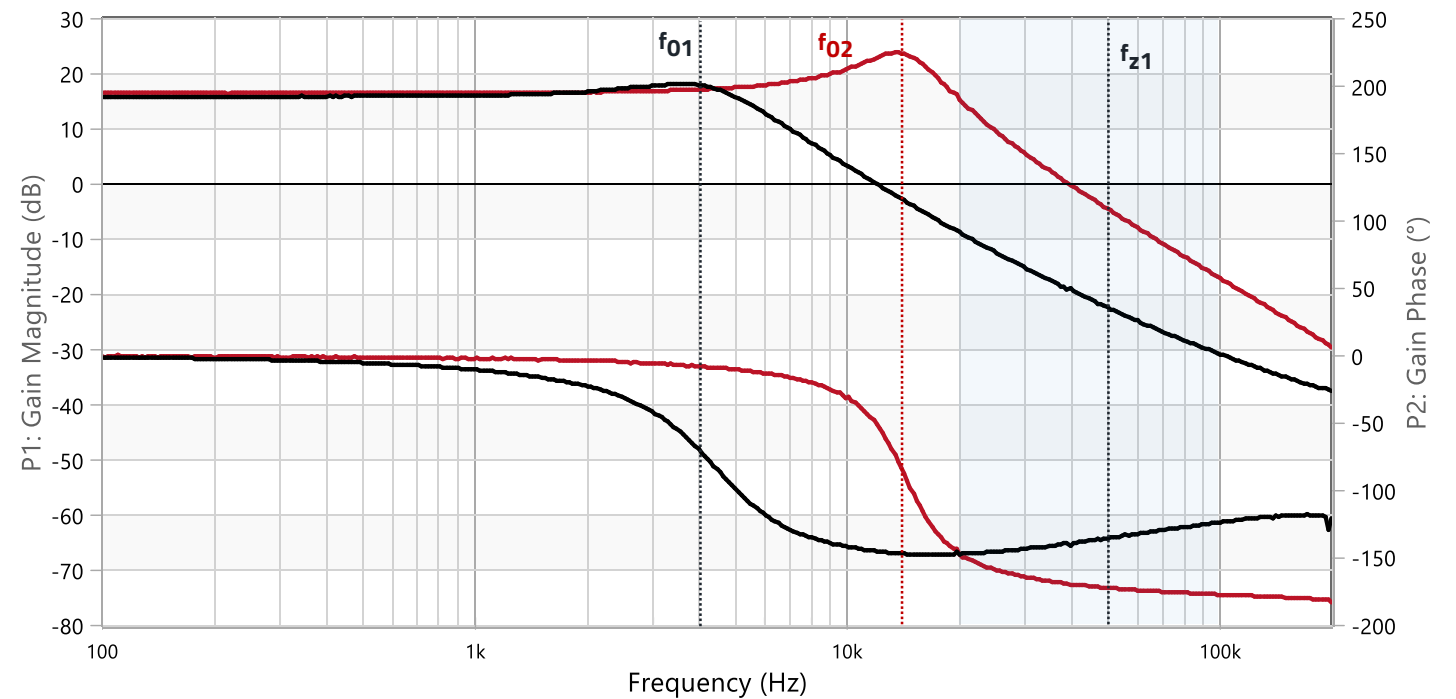

DESIGN CASE EXAMPLE: IMPACT OF BULK CAPACITOR

How did the plant response change?

Plant TF with **Co1+Co2**

$$f_{z1} \approx 50 \text{ kHz}$$

$$f_{o1} \approx 4 \text{ kHz}$$

$$Q_1 \approx 1.2$$

Plant TF with **Co1**


$$f_{z2} \approx 8 \text{ MHz}$$

$$f_{o2} \approx 14 \text{ kHz}$$

$$Q_2 \approx 2.5$$

Fixed compensator-1, Co2 removed ...

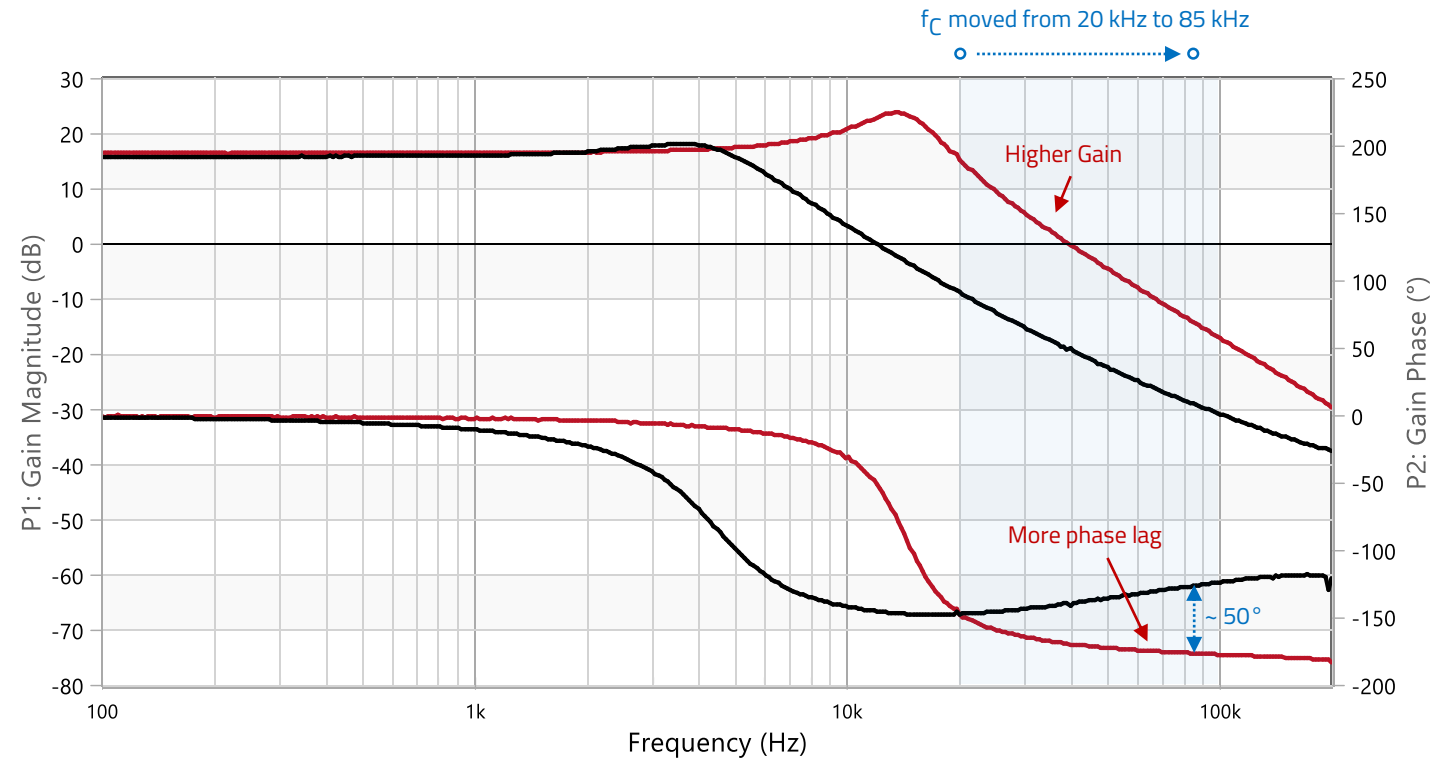- Higher gain \rightarrow Higher crossover f_c
- Higher crossover:
 - Higher phase lag (no ESR zero)
 - Compensator:
 - Maximum phase lead at 20 kHz
 - Lower phase lead at 85 kHz




DESIGN CASE EXAMPLE: IMPACT OF BULK CAPACITOR


Compensator redesign for stability without Co2

Compensator-2 circuit component values:

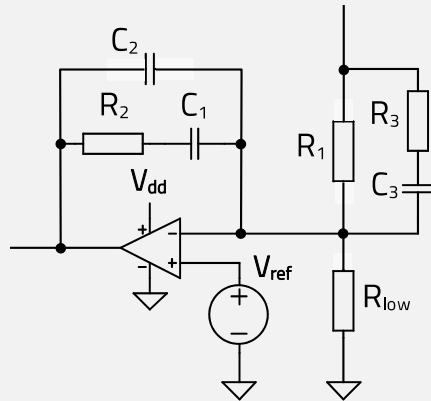- $R_1 = 73.2 \text{ k}\Omega$
- $R_{\text{low}} = 10 \text{ k}\Omega$
- $R_2 = 4.7 \text{ k}\Omega$
- $R_3 = 4.7 \text{ k}\Omega$
- $C_1 = 6.8 \text{ nF}$
- $C_2 = 470 \text{ pF}$
- $C_3 = 330 \text{ pF}$



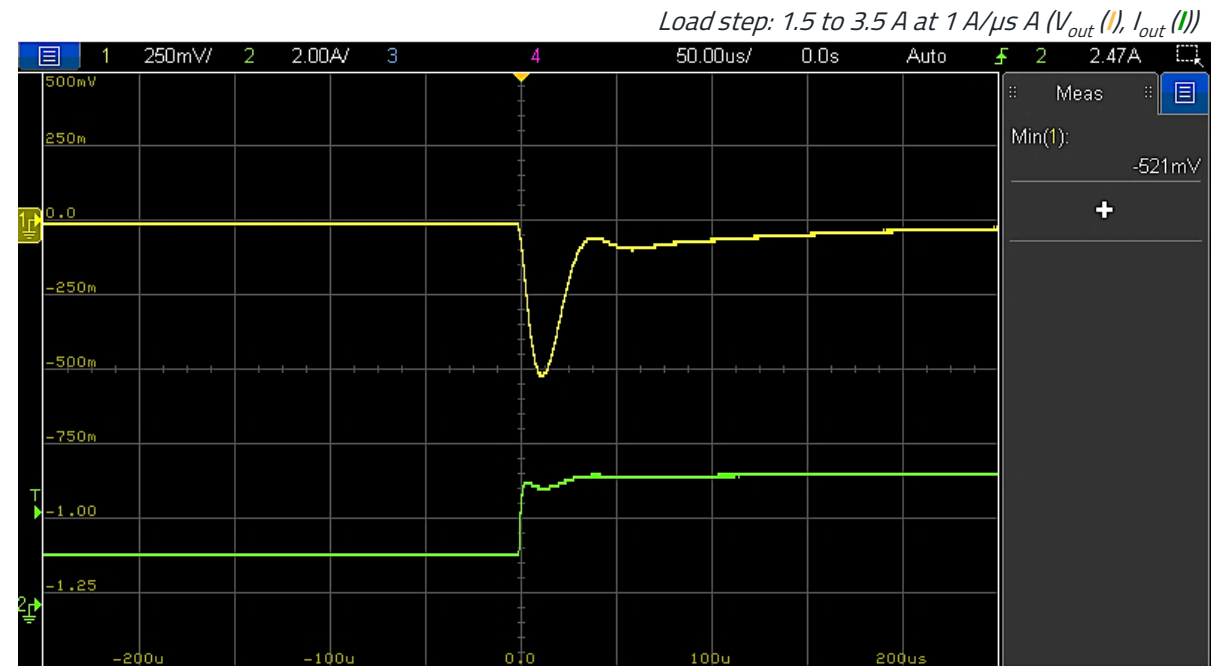$f_c \approx 21 \text{ kHz}$, $PM \approx 59.8^\circ$ and $GM \approx 18 \text{ dB}$



Stable, but much higher undershoot (0.52 V) due to no bulk capacitor ...

DESIGN CASE EXAMPLE: SAME CAPACITANCE - DIFFERENT ESR


DESIGN CASE EXAMPLE: IMPACT OF ESR

Specification and output capacitors

- $V_{in} = 12\text{ V}$
- $V_{out} = 3.3\text{ V}$
- $I_{out} = 4\text{ A}$
- $F_{sw} = 400\text{ kHz}$
- $L = 4.7\text{ }\mu\text{H}$ (MAPI 74438367047)
- $\Delta V_{out} < 0.4\%$ of V_{out} (i.e. 20 mV)
- Use same C_{o1} for ΔV_{out} as previous design

- Bulk capacitor (C_{o3}):
 - WCAP-ATLI 860080474010
 - 220 μF , 25 V, 75 m Ω (@ 30 kHz)

REDEXPERT DATA: WCAP-ATLI 860080474010

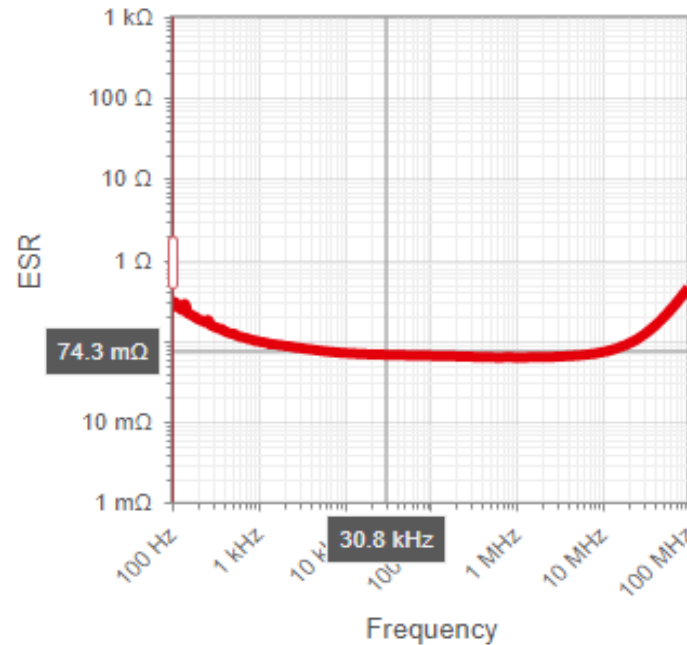

Aluminum electrolytic capacitor




DESIGN CASE EXAMPLE: IMPACT OF ESR


Open-loop response and stability margins: Co1+Co3 and compensator-3

Compensator-3 design ($f_c=30$ kHz, $PM>50^\circ$)

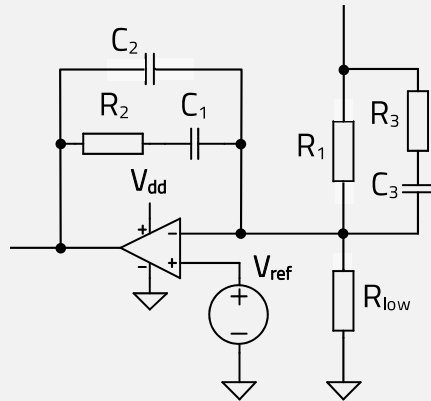- $R_1 = 45.5$ k Ω
- $R_{low} = 10$ k Ω
- $R_2 = 73.2$ k Ω
- $R_3 = 13$ k Ω
- $C_1 = 150$ pF
- $C_2 = 33$ pF
- $C_3 = 100$ pF



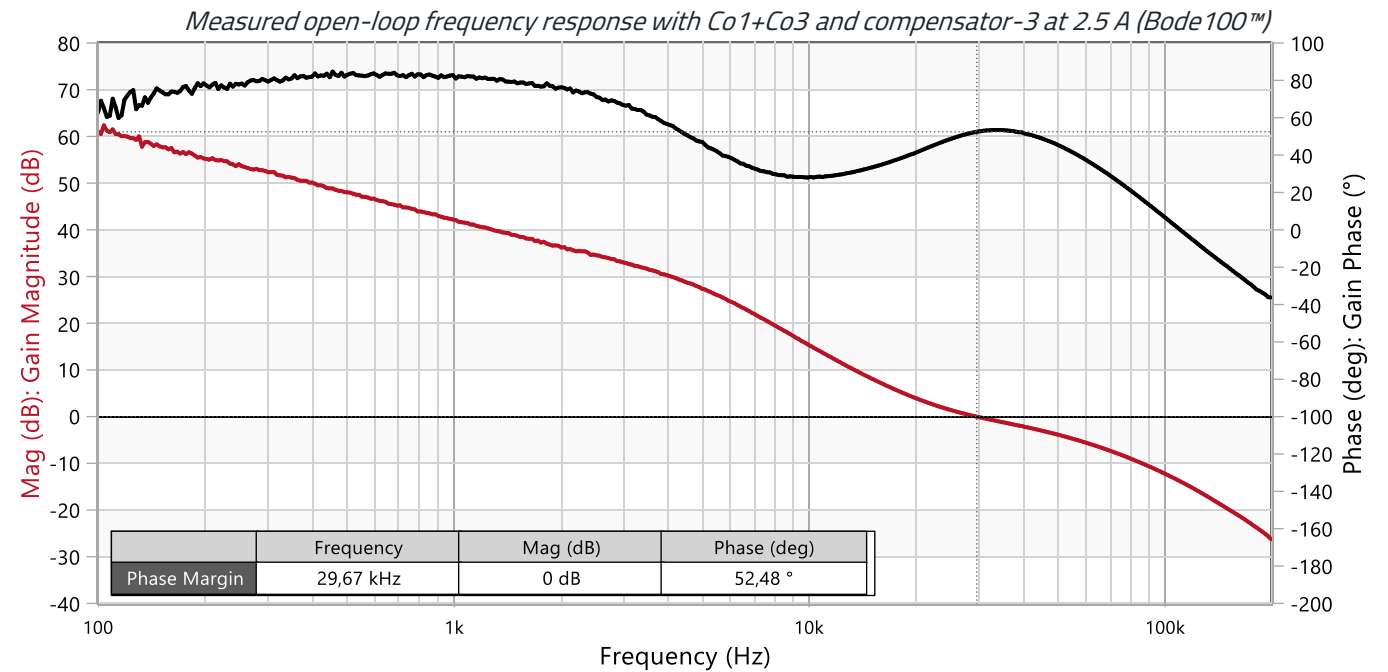$f_c \approx 30$ kHz, $PM \approx 52.5^\circ$ and $GM \approx 15$ dB




DESIGN CASE EXAMPLE: IMPACT OF ESR


Transient response with Co1+Co3 and compensator-3

Compensator-3 circuit component values:

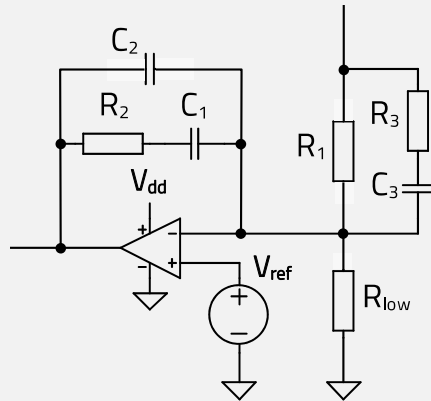- $R_1 = 45.5 \text{ k}\Omega$
- $R_{\text{low}} = 10 \text{ k}\Omega$
- $R_2 = 73.2 \text{ k}\Omega$
- $R_3 = 13 \text{ k}\Omega$
- $C_1 = 150 \text{ pF}$
- $C_2 = 33 \text{ pF}$
- $C_3 = 100 \text{ pF}$



Undershoot ~ 85 mV

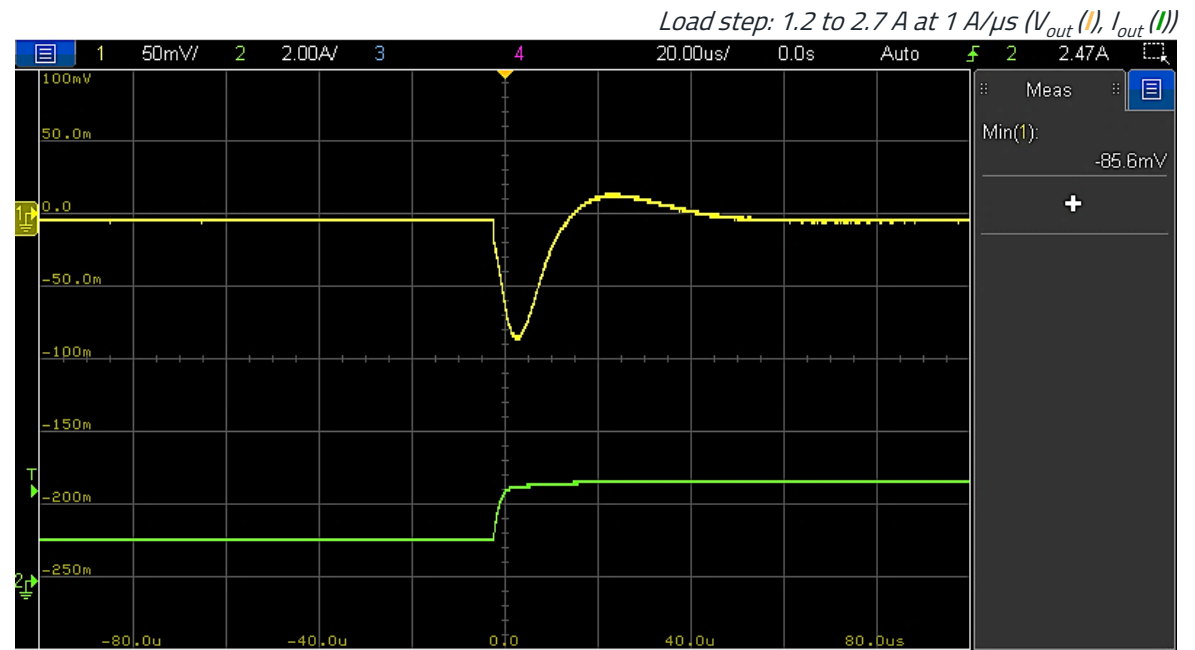

DESIGN CASE EXAMPLE: IMPACT OF ESR

Replacing Co3 by an equivalent SMD, low-profile part (Co4)


Typical requirements change:

- THT to SMT
- Mechanical constraints
- Stock availability
- Cost reduction


Example: All-SMT, Max. Height 4 mm

- Co4: WCAP-PHGP 875015119006
 - H-chip polymer, SMT, height: 2 mm
 - 220 μ F, 6.3 V, 6 m Ω (@ 30 kHz)
- Co3 replaced by Co4

REDEXPERT DATA: WCAP-PHGP 875015119006

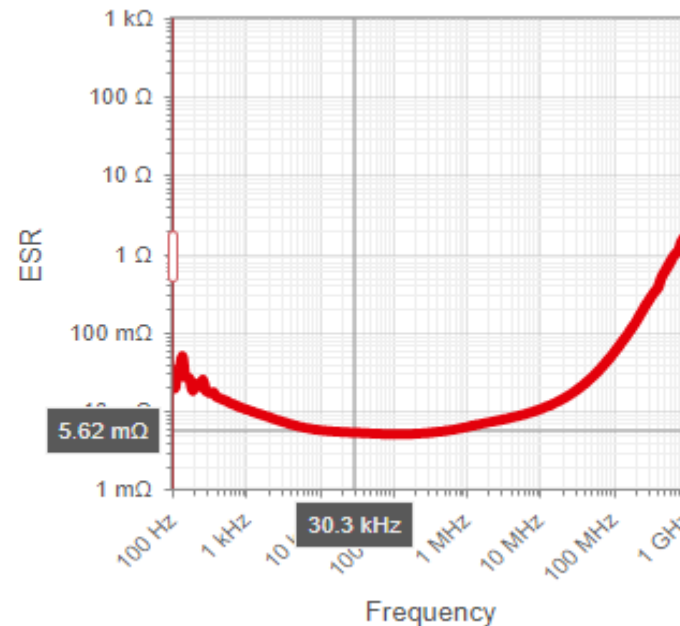


H-chip polymer capacitor

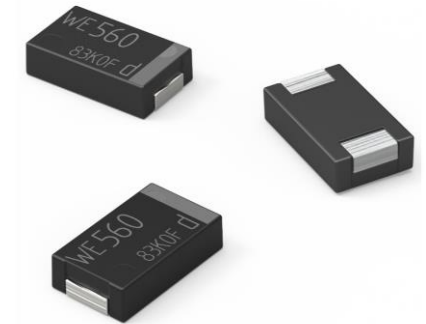


DESIGN CASE EXAMPLE: IMPACT OF ESR

Buck converter board and open-loop response with Co1+Co4 and compensator-3

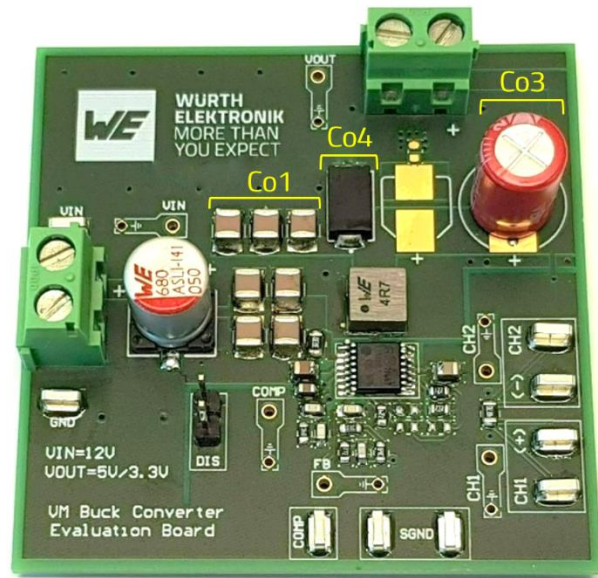

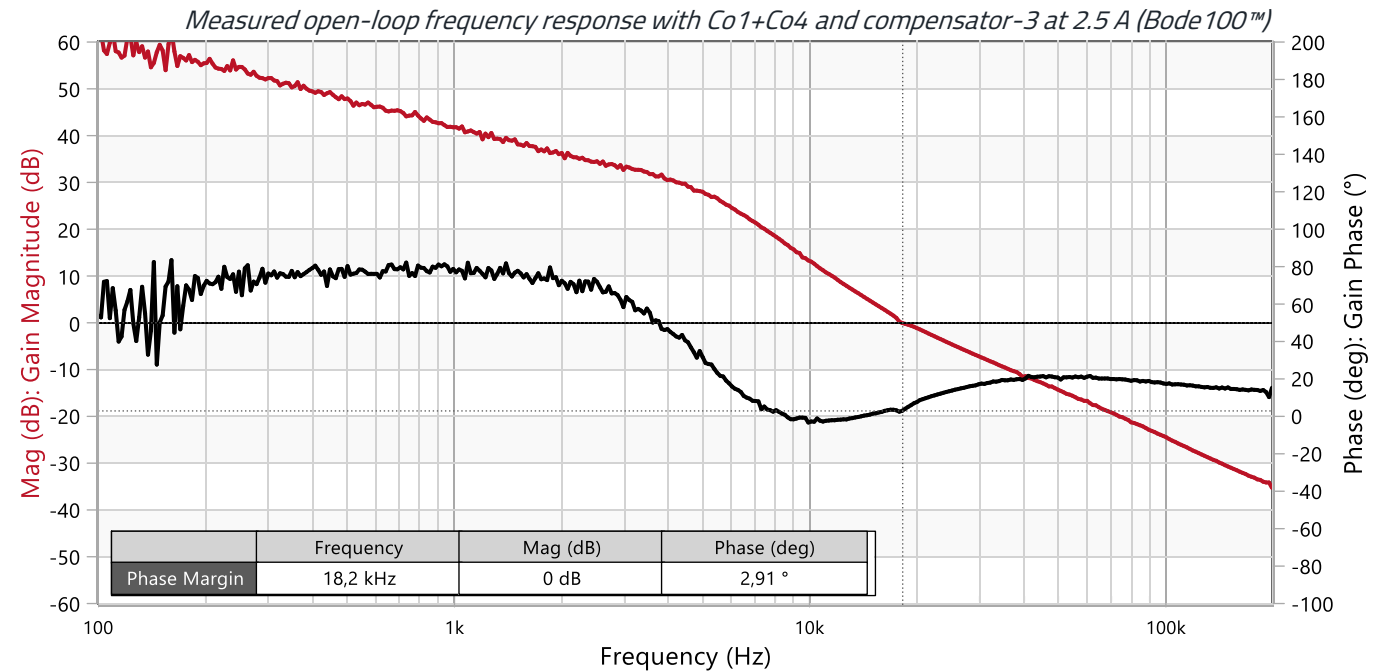Prototype VM-CCM buck board with Co1, Co3 and Co4




PM below 10° - On the brink of instability !

DESIGN CASE EXAMPLE: IMPACT OF ESR

Small load transient steps


Small load transient step:

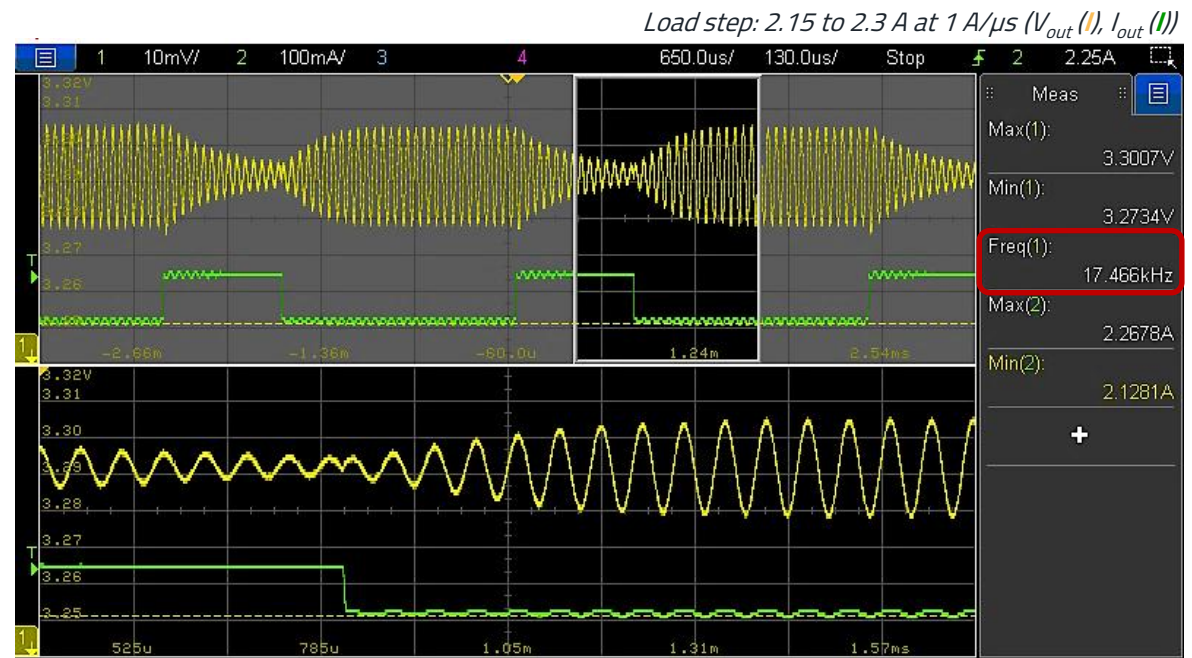- From 2.15 A to 2.3 A
- Load step up: decaying oscillation
- Load step-down: permanent oscillation
- Above ~ 2.2 A \rightarrow Stable
- Below ~ 2.2 A \rightarrow Unstable
- Oscillation frequency ≈ 17.5 kHz
- Remember OL crossover $f_c \approx 18$ kHz




DESIGN CASE EXAMPLE: IMPACT OF ESR

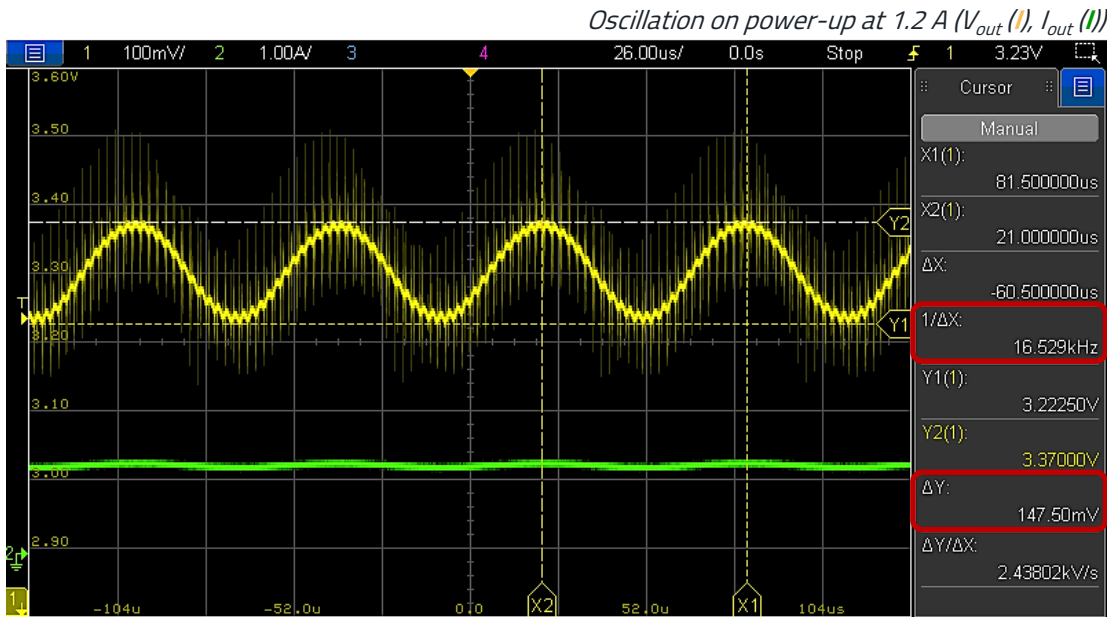Power-up at 1.2 A load: Oscillation and erratic behavior



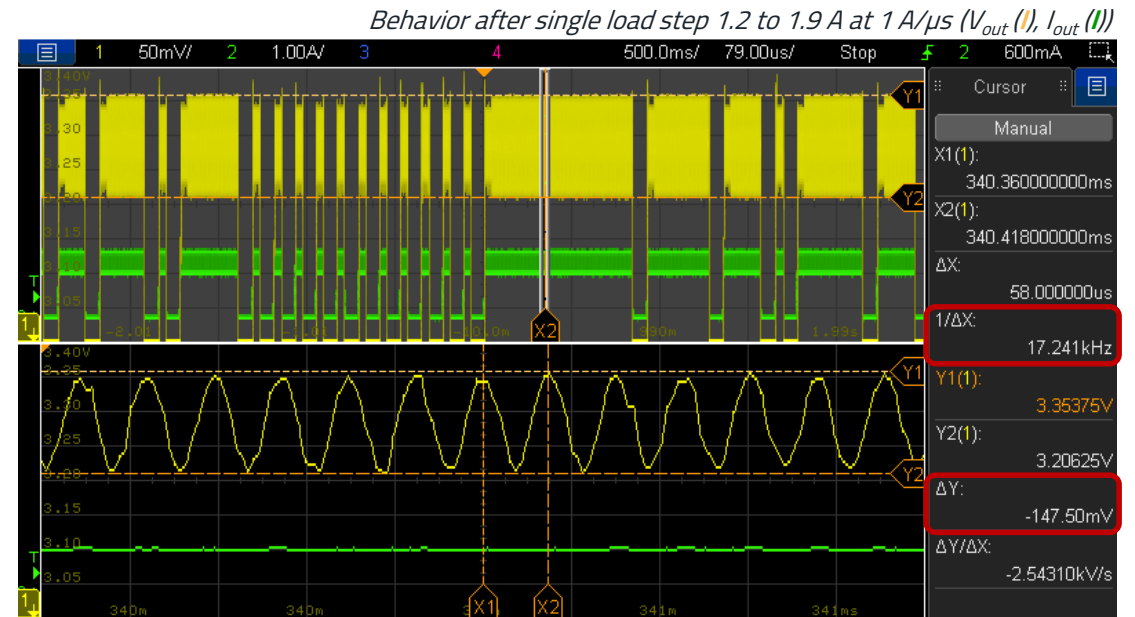Unstable operation at constant 1.2 A load
Oscillation at ~ 16.5 kHz with amplitude ~ 150 mV



Erratic behavior after a small load transient applied
Oscillation at ~ 17 kHz with amplitude ~ 150 mV

DESIGN CASE EXAMPLE: IMPACT OF ESR

How did the plant response change?

Plant TF with **Co1+Co3**

$f_{z1} \approx 9 \text{ kHz}$


Plant TF with **Co1+Co4**

$f_{z2} \approx 100 \text{ kHz}$

- f_0 and Q are similar

Replacing Co3 by Co4 ...

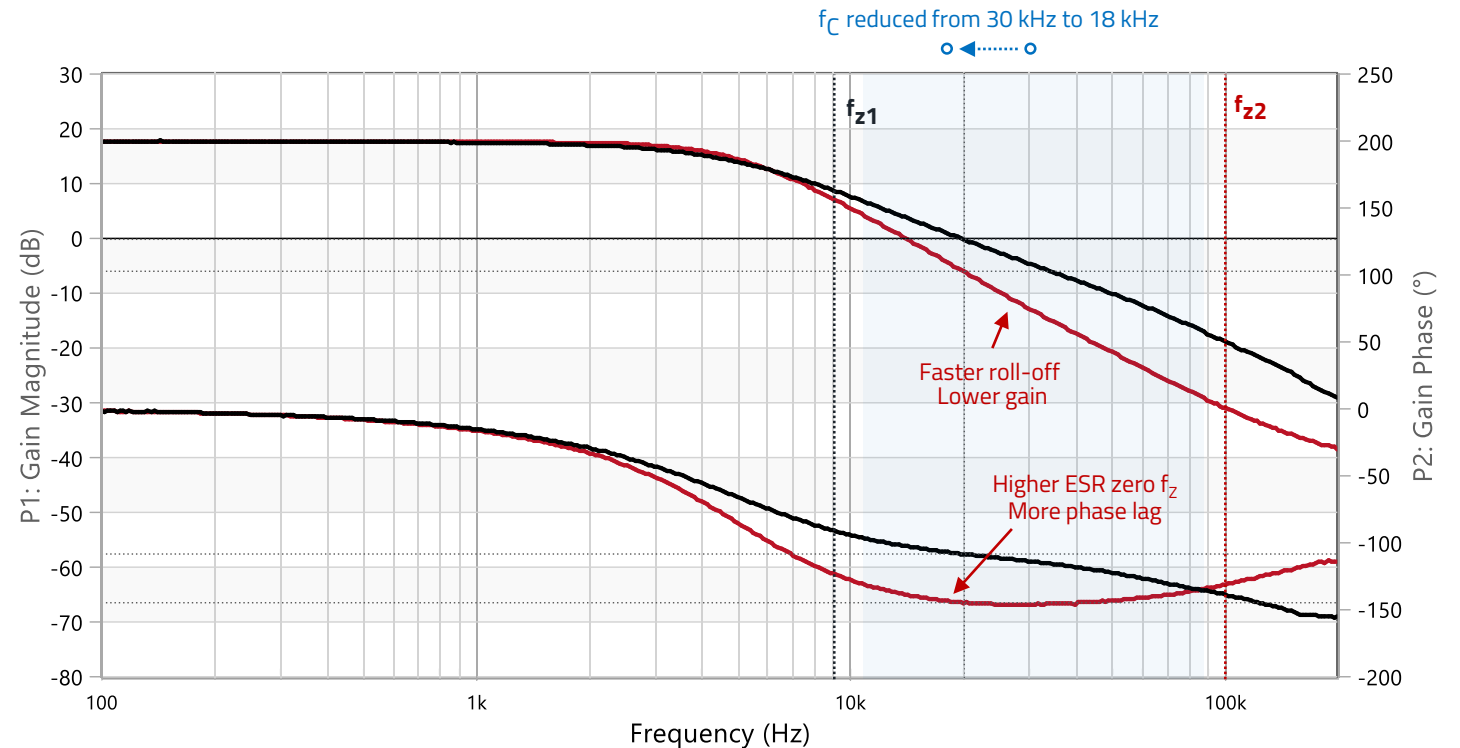- Lower gain \rightarrow Lower crossover f_c
- Lower crossover (18 kHz):
 - Higher phase lag (higher f_z)
 - Compensator:
 - Lower phase lead at 18 kHz




DESIGN CASE EXAMPLE: IMPACT OF ESR


Compensator redesign for stability with Co1+Co4

Compensator-4 circuit component values:

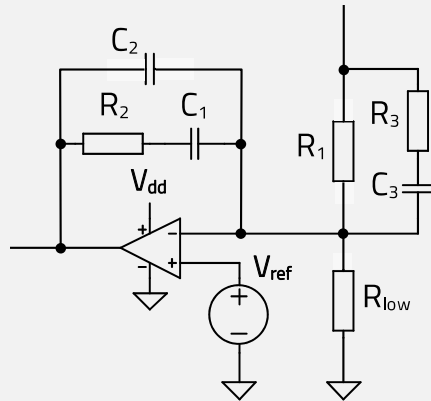- $R_1 = 45.5 \text{ k}\Omega$
- $R_{\text{low}} = 10 \text{ k}\Omega$
- $R_2 = 73.2 \text{ k}\Omega$
- $R_3 = 2.7 \text{ k}\Omega$
- $C_1 = 220 \text{ pF}$
- $C_2 = 33 \text{ pF}$
- $C_3 = 330 \text{ pF}$



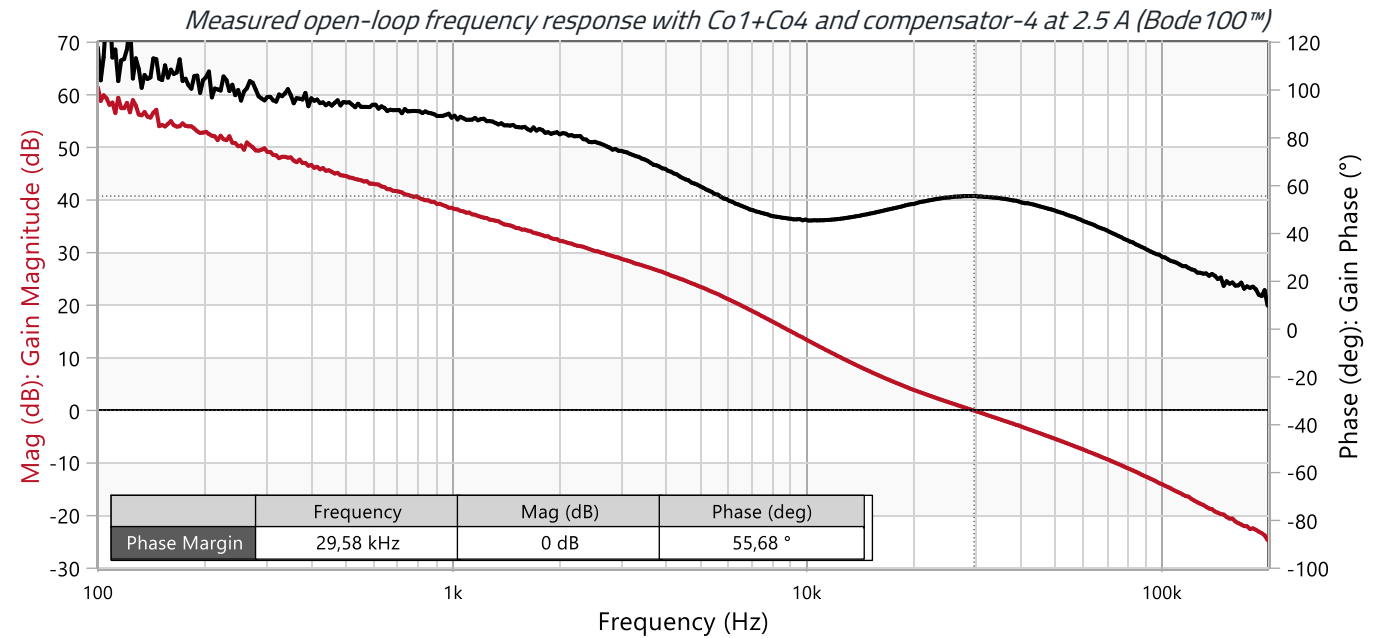$f_c \approx 30 \text{ kHz}$, $PM \approx 55^\circ$ and $GM \approx 25 \text{ dB}$




DESIGN CASE EXAMPLE: IMPACT OF ESR


Transient response with Co1+Co4 and compensator-4

Compensator-4 circuit component values:

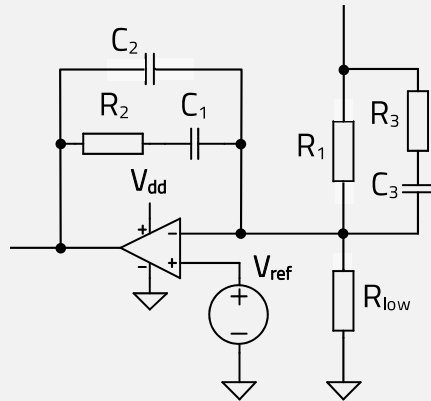- $R_1 = 45.5 \text{ k}\Omega$
- $R_{\text{low}} = 10 \text{ k}\Omega$
- $R_2 = 73.2 \text{ k}\Omega$
- $R_3 = 2.7 \text{ k}\Omega$
- $C_1 = 220 \text{ pF}$
- $C_2 = 33 \text{ pF}$
- $C_3 = 330 \text{ pF}$



Undershoot ~ 45 mV

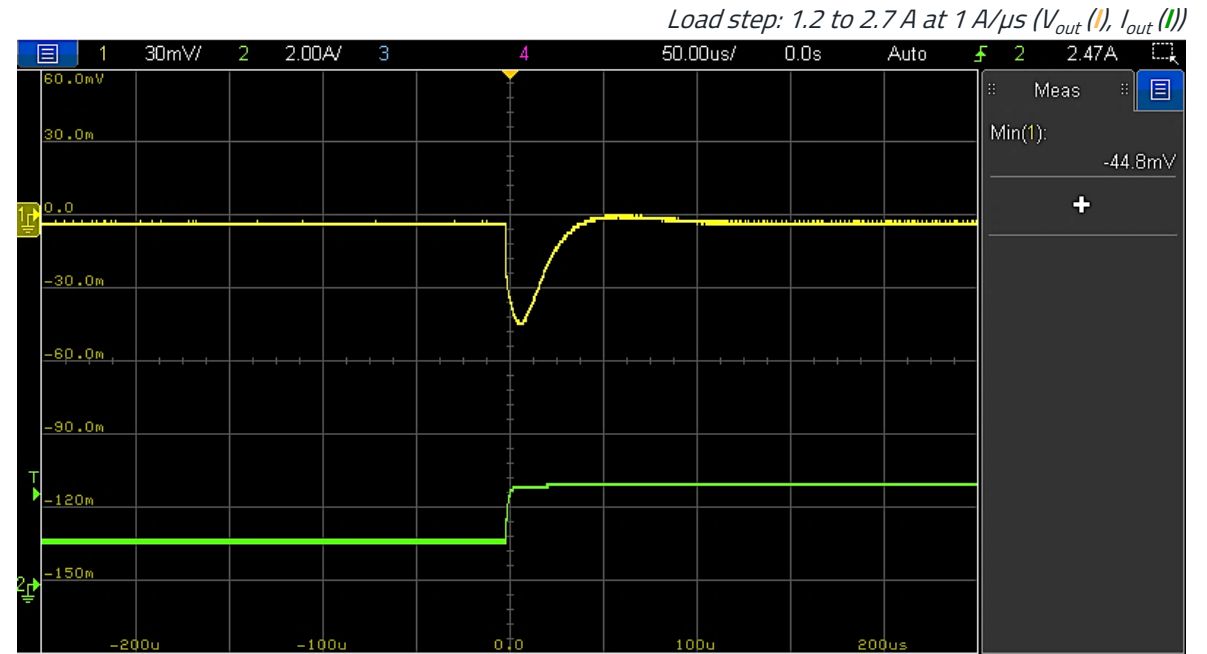

Lower undershoot than Co3, thanks to lower ESR

A STABLE CONTROL LOOP FOR A WIDE RANGE OF OUTPUT CAPACITORS?

A STABLE CONTROL-LOOP FOR ANY OUTPUT CAPACITOR?


The plant response with different capacitors

Co1 only

Co1+Co2

Co1+Co3

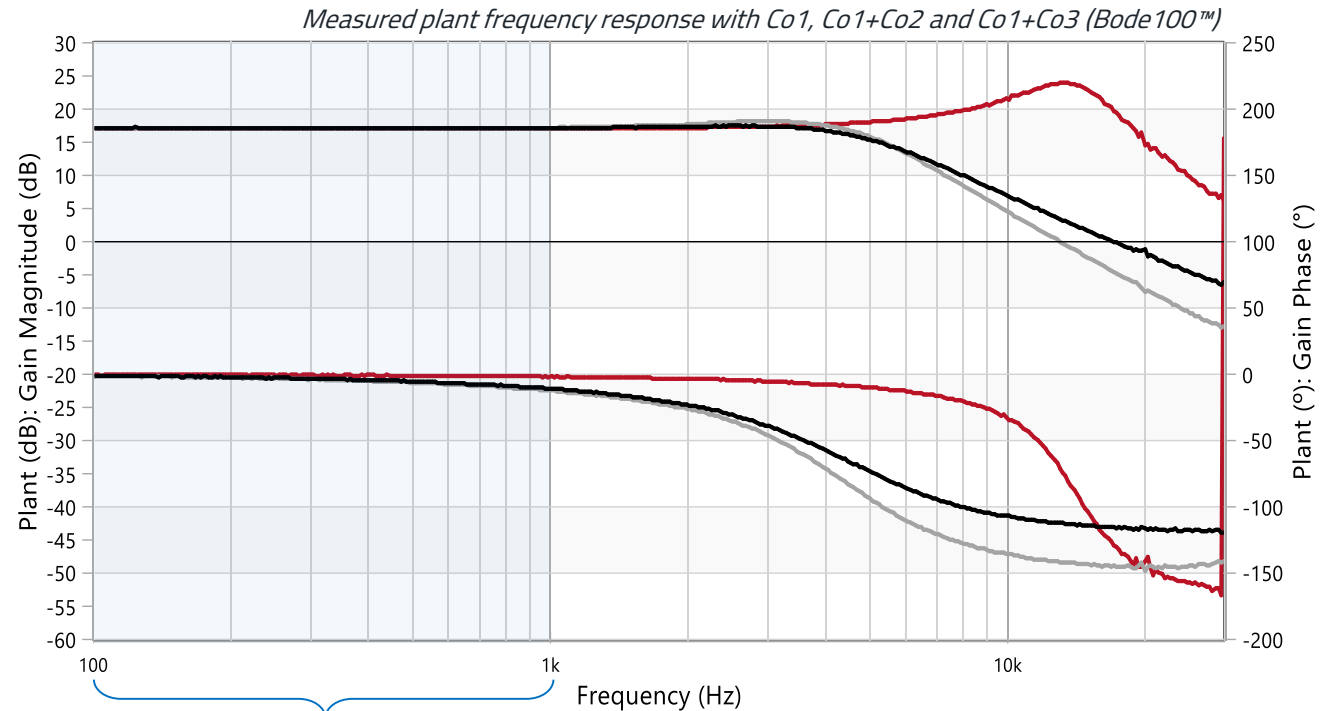- Co4 not shown → Very similar to Co2
- Below $f \approx 1$ kHz:
 - Plant dominated by $G_0 \approx 17$ dB (≈ 7)
 - No effect of f_0 and f_z
 - Little to no phase lag
- **What if we select f_c below 1 kHz?**




A STABLE CONTROL-LOOP FOR ANY OUTPUT CAPACITOR?

A type-1 compensator for 1 kHz crossover frequency


- Type-1 Compensator
- Integrator C_1 - R_1
- High DC-gain
- No phase lead
- Phase margin $\sim 90^\circ$

- R_1 and R_{low} set $V_{out}=5\text{ V}$
- C_1 calculated for $f_c=1\text{ kHz}$:
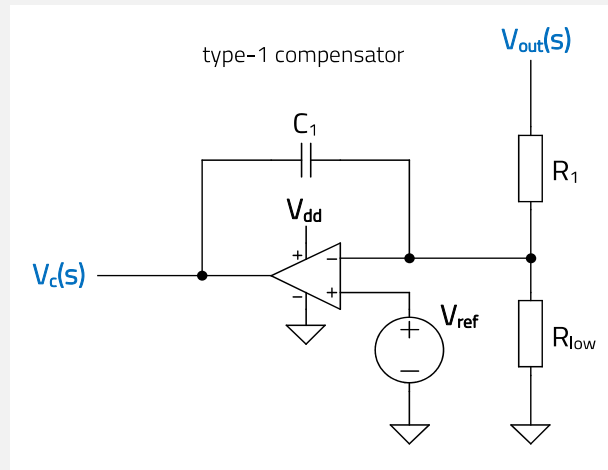
$$C_1 \approx \frac{G_0}{2 \cdot \pi \cdot f_c \cdot R_1} = \frac{7}{2 \cdot \pi \cdot 1\text{k} \cdot 73.2\text{k}} \approx 15\text{ nF}$$




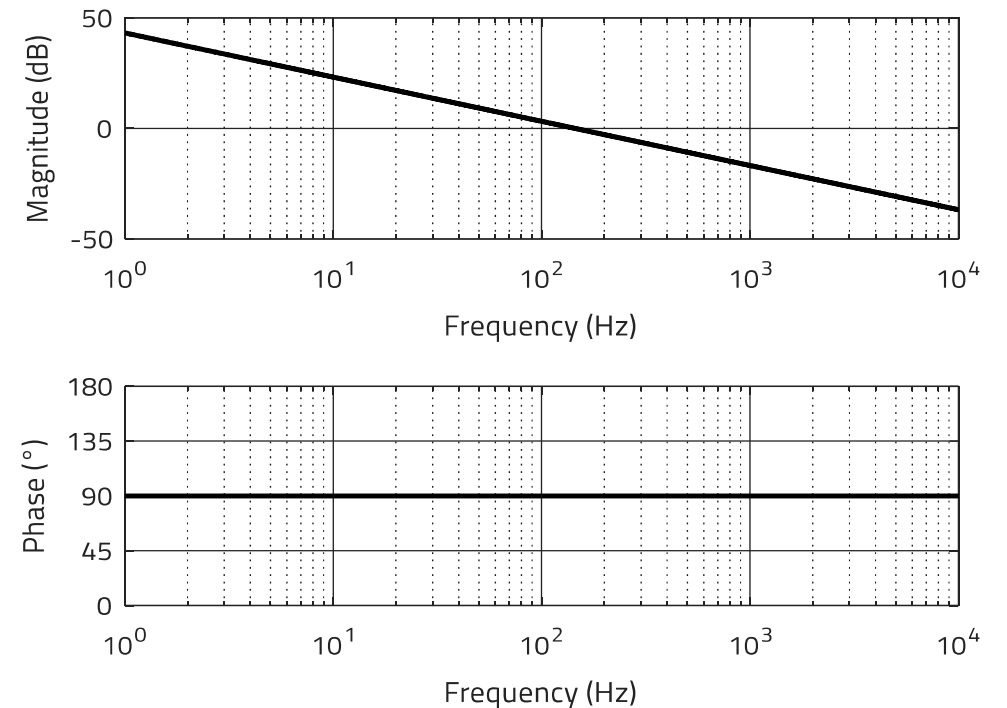Type-1 compensator frequency response with $R_1=73.2\text{ k}\Omega$ and $C_1=15\text{ nF}$ (MATLAB™)




A STABLE CONTROL-LOOP FOR ANY OUTPUT CAPACITOR?

Open-loop response and phase margin

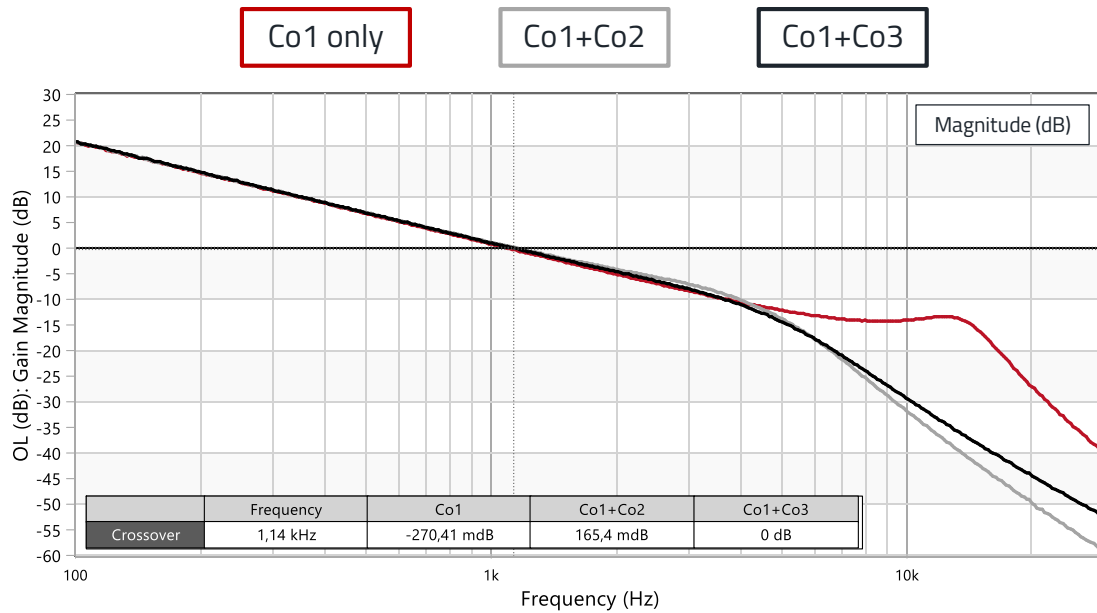

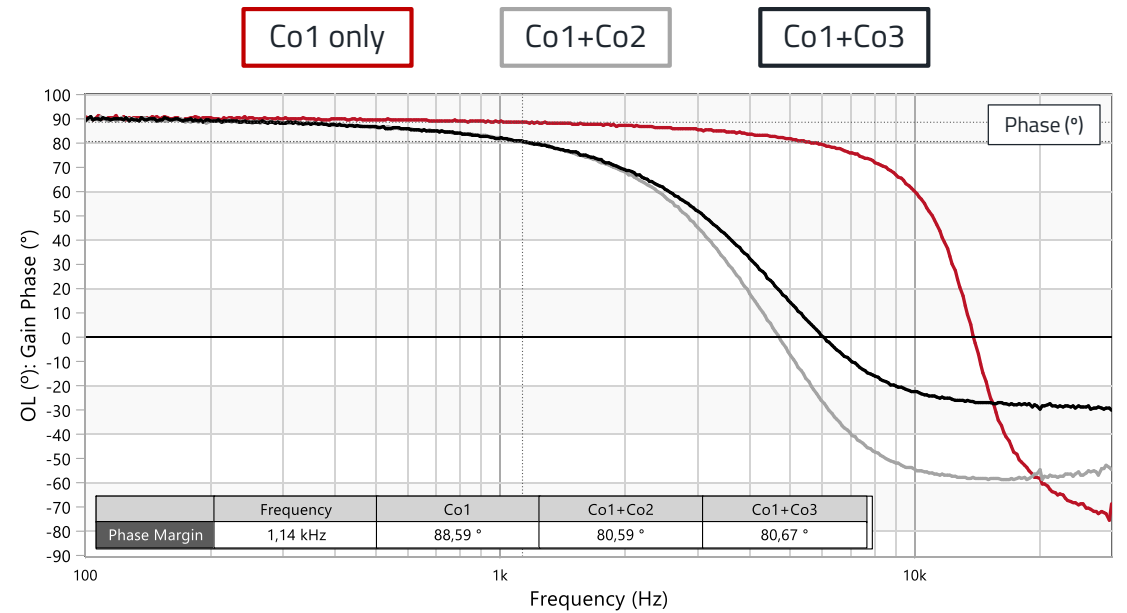Crossover frequency $f_c \sim 1$ to 1.2 kHz




Minimum phase margin $\sim 80^\circ$




A STABLE CONTROL-LOOP FOR ANY OUTPUT CAPACITOR?

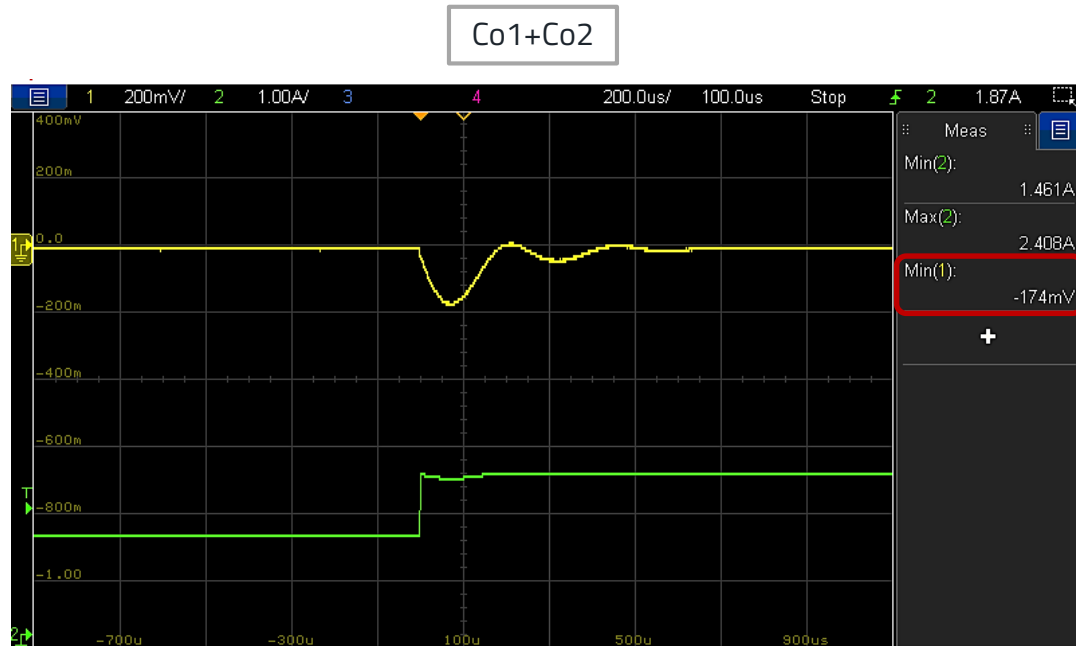Transient response for Co2 and Co3 cases with type-1 compensator



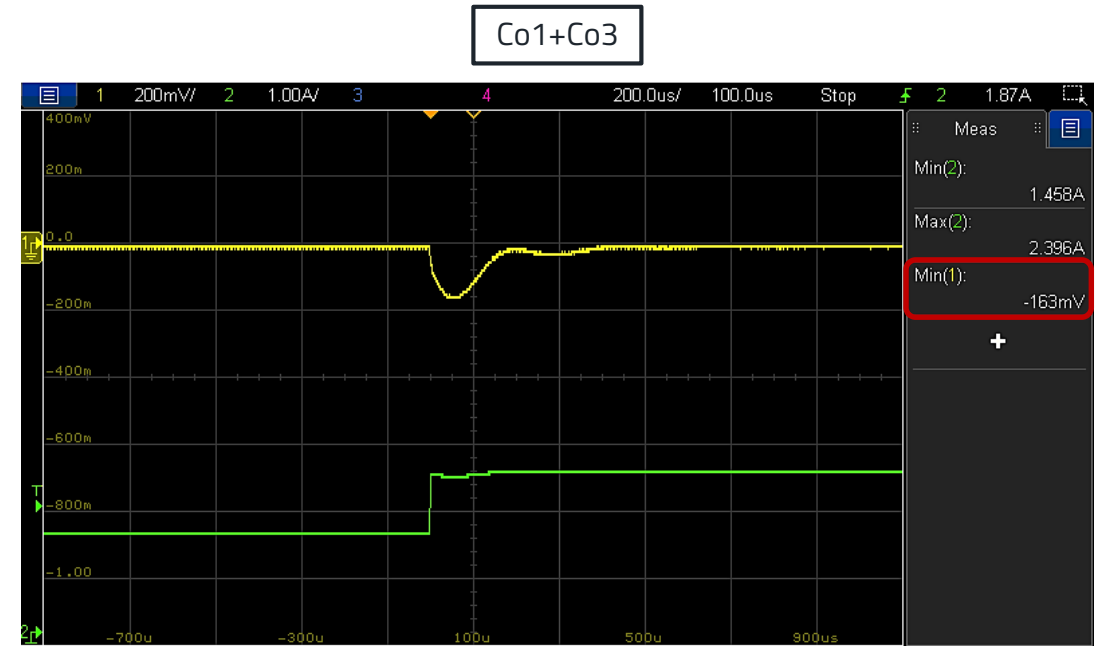Load step: 1.2 to 2.4 A at 1 A/ μ s (V_{out} (I), I_{out} (II))




Load step: 1.2 to 2.4 A at 1 A/ μ s (V_{out} (I), I_{out} (II))


Despite smaller load step: longer settling time and higher undershoot than before. Degraded transient performance. There is a small underdamped oscillation with Co2 and not with Co3, despite same phase margin $\sim 80^\circ$... Let us see ...

A STABLE CONTROL-LOOP FOR ANY OUTPUT CAPACITOR?

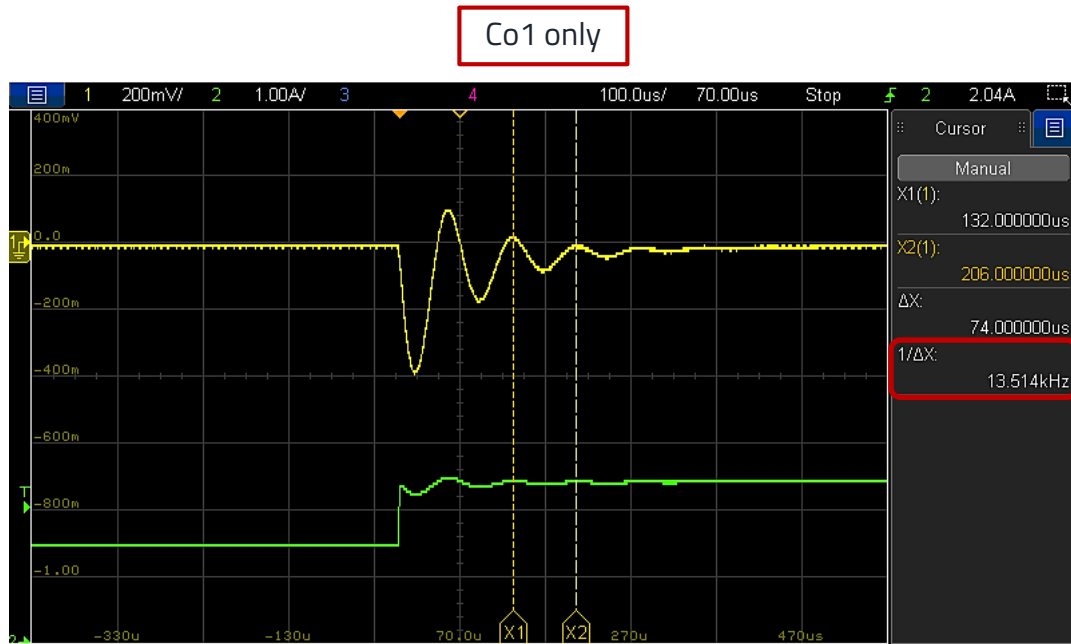Transient response for Co1-only case: underdamped oscillation despite high phase margin



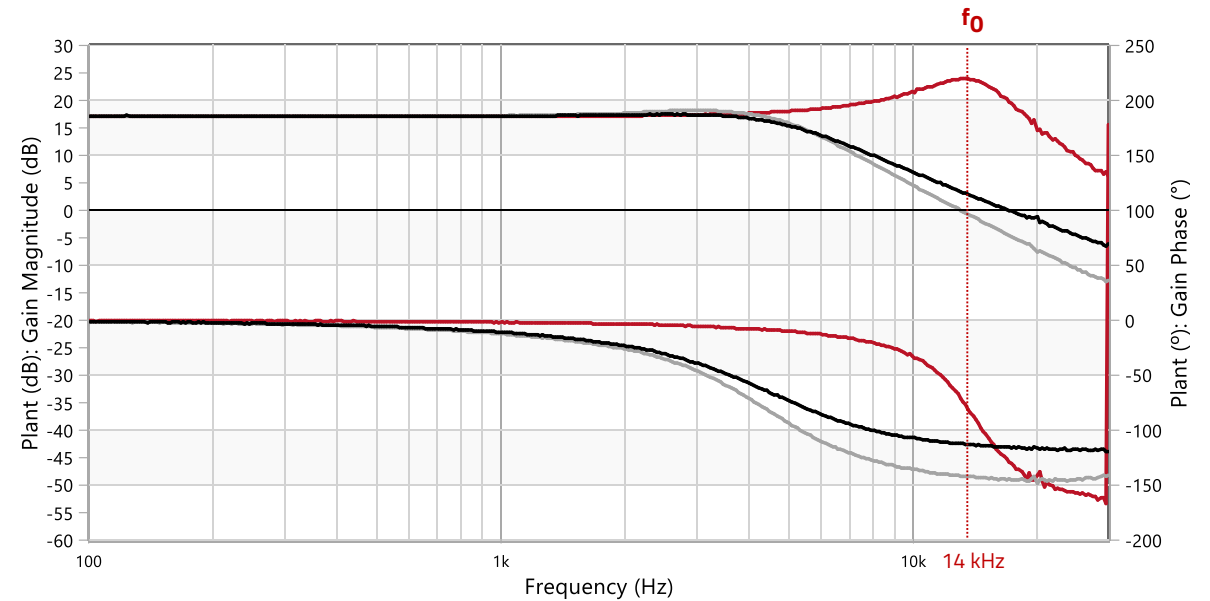Load step: 1.2 to 2.4 A at 1 A/μs ($V_{out}(t)$, $I_{out}(t)$)




Stable, but with some underdamped oscillation at ~ 14 kHz
LC resonant double-pole with **Co1-only** is at ~ 14 kHz with a Quality factor ~ 2.5

A STABLE CONTROL-LOOP FOR ANY OUTPUT CAPACITOR?

Lack of gain of control system above crossover

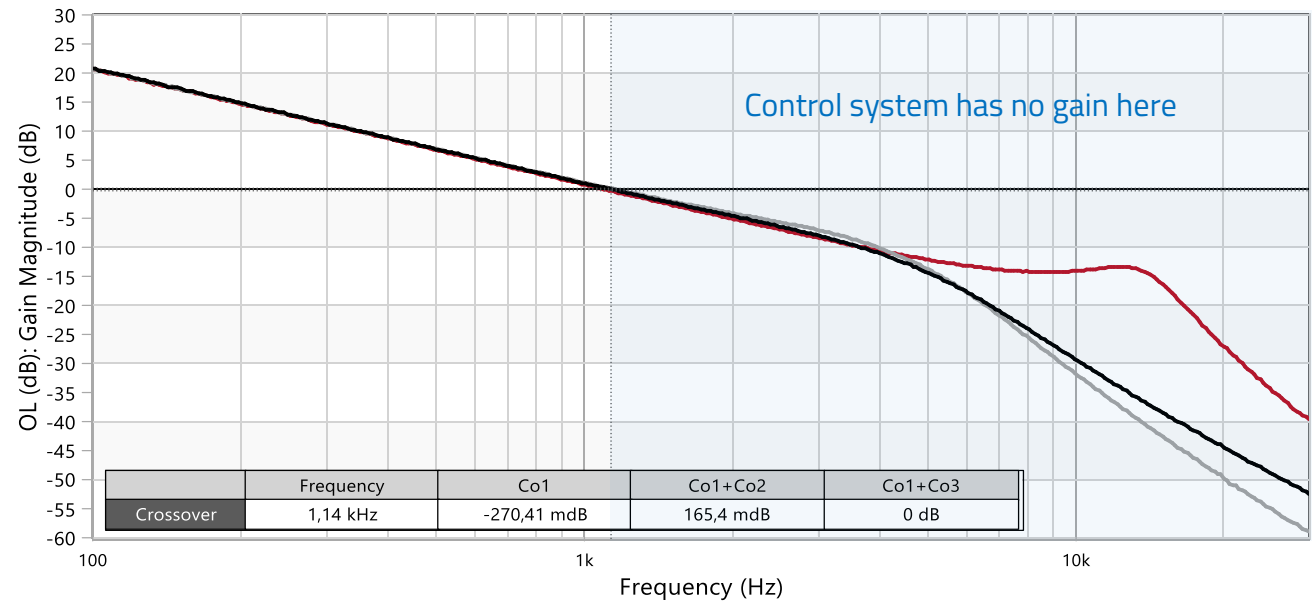- Closed-loop bandwidth $f_{C_CL} \approx f_{C_OL}$
- No gain above f_C
- System cannot correct for oscillations above f_C
- Issues for high Q (underdamped double-pole)
- Very high Q \rightarrow Could cross over again at 0 dB !
- Must be careful with Q if using this approach!



SUMMARY - KEY TAKEAWAYS

SUMMARY AND KEY TAKEAWAYS

- Output capacitor(s) parameters shape the converter plant transfer function: Capacitance and ESR values
- For a fixed compensator, changes in the output capacitors will affect the stability margins
- Transient performance degradation and even full-blown instability are possible
- Always check feedback loop stability margins after changes in output capacitor(s)
- Redesign compensator to keep good stability margins
- Very-low crossover frequency: stability for many different output capacitor and power inductors
- But ... degraded transient response and oscillation for high quality factors
- A compensator tailored to a specific plant characteristic will provide the best performance



THANK YOU FOR YOUR ATTENTION!